

# Basic OP-Amp circuits

## Practical exercise in Analog Electronics

### *Abstract*

*In this lab the most basic OP-Amp circuits should be connected and characterized. Some fundamental non ideal properties of the OP-Amp will also be characterized.*




## 1 Basic OP Amp circuits

In this lab the most commonly used OP circuits should be connected, measured on and analyzed. The influence of some of the non-ideal properties of the OP-Amp is also investigated.
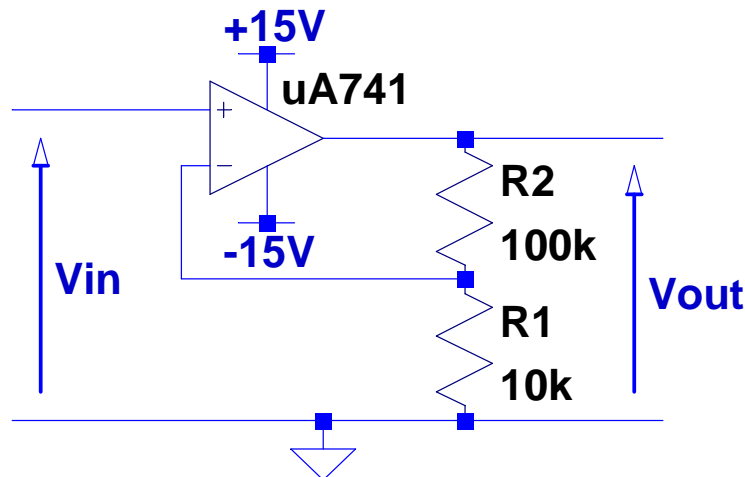
### 1.1 Non Inverting Amplifier and Frequency response


With this circuit the non inverting amplifier should be characterized and verified and the frequency response should be characterized.



- Connect the non inverting amplifier according to the figure
- Connect the signal generator to  $V_{in}$ . Set the amplitude to 100mV peak-to-peak and the frequency to 500 Hz.
- Connect the oscilloscope probes to  $V_{in}$  (Ch1) and  $V_{out}$  (Ch2).
  - Calculate the theoretical amplification and verify that against measurements.
- Set the oscilloscope in XY-mode.
  - Draw  $V_{out}=f(V_{in})$ . Explain what you see.
- Set the oscilloscope in normal (timebase) mode.
- Sweep the frequency from 1Hz and until the gain drops to zero for the values 1, 2, 5, 10, 20, 50, 100,... Hz.
  - Draw the transfer function  $H(f)$ . Use a dB scale for the y-axis and a logarithmic frequency scale.
  - Determine the cut-off frequency,  $f_c$  and the unit gain frequency  $f_T$  from the graph. Compare with theoretical values.
- Draw the waveform for  $V_{out}=f(t)$  at the cut-off frequency, normalize the amplitude to 1.
- Draw  $V_{out}=f(V_{in})$  using the XY-mode for the same frequency.
- Increase the input voltage to 200mV peak-to-peak.
- Repeat the frequency sweep as above.
  - Draw all the three graphs as above in the same diagram as before.
  - Determine the cut-off frequency and compare with theoretical value.
- Explain the results you have achieved. Comment observed difference in all graphs.
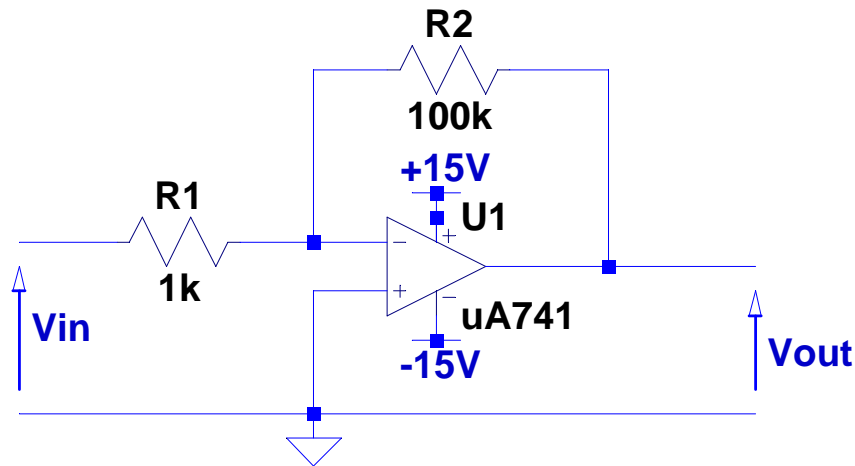
### 1.2 Inverting Amplifier and Offset compensation


With this circuit the inverting amplifier and the influence of off-set should be studied.



- Connect the inverting amplifier according to the figure
- Calculate the theoretical gain and verify it against the measured gain. Present both values.
- Ground  $V_{in}$  and measure  $V_{out}$ .
  - Explain by theoretical calculations which offset are dominating,  $V_{IO}$  or  $I_{IO}$  and present the values using the values given in the data-sheet.
- Compensate the offset by adding an external potentiometer according to the data-sheet.
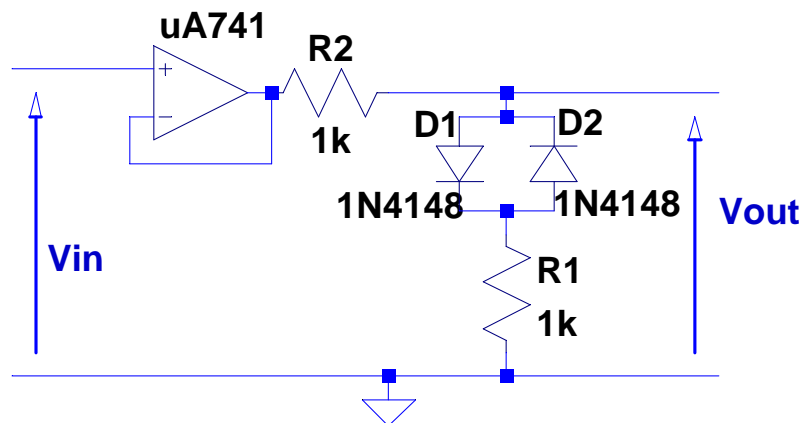
### 1.3 Voltage follower and feed-back

This circuit uses a voltage follower driving a non-linear circuit. Feed-back should be used to improve the linearity for the circuit.



- Connect the voltage follower with additional load circuit according to the figure
- Connect the signal generator to  $V_{in}$ . Set the amplitude to 5V peak-to-peak and the frequency to 500 Hz.
- Draw the waveform for  $V_{in}=f(t)$  and  $V_{out}=f(t)$ .
- Draw  $V_{out}=f(V_{in})$  using the XY-mode for the same frequency.
- Use the principle of feed-back to eliminate the nonlinear response.
- Draw the waveform and  $V_{out}=f(V_{in})$  in the same graphs as before.

## 2 Documentation

The lab should be documented as a in word or some other word-processor. Graphs for  $H(f)$  should be computer generated with either excel, Matlab or software you choose. Graphs which is copied from the oscilloscope can either be hand-drawn, photographed or drawn in some software.

Good Luck  
/Kent