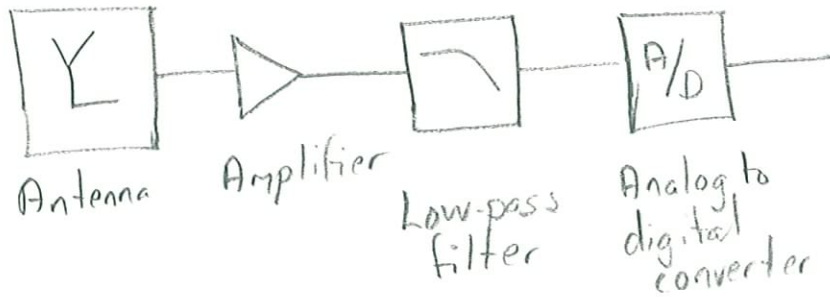


Analog electronics


Electronic systems can be described by a block diagram



Filter

Circuit that let some frequencies pass and stops other

Low pass

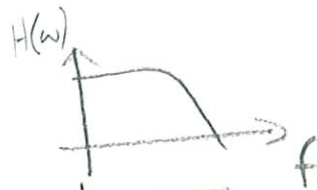


High pass



Band pass



Band stop

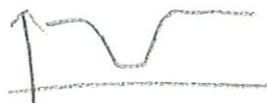



Impedance
 $Z = R$



$$Z = \frac{1}{j\omega C}$$




$$Z = j\omega L$$

The same calculations can be used for impedances as resistances




$$Z = Z_R + Z_L = R + j\omega L$$

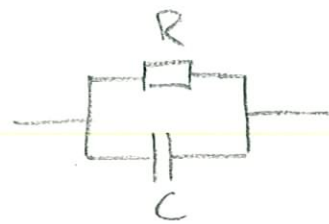

$$Z = Z_R // Z_C = \frac{Z_R \cdot Z_C}{Z_R + Z_C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$$

RC-filter

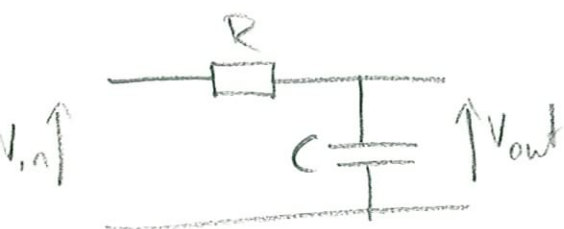

Voltage division

$$\Rightarrow V_{out} = V_{in} \frac{Z_C}{Z_R + Z_C} = V_{in} \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$V_{out} = V_{in} \frac{1}{1 + j\omega RC}$$

Transfer function $H(\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\frac{\omega}{\omega_0}} = \frac{1}{1 + j\frac{f}{f_0}}$


Where ω_0 or f_0 is the cut-off frequency.

$$|H(\omega_0)| = \frac{1}{\sqrt{1 + (\frac{\omega_0}{\omega_0})^2}} = \frac{1}{\sqrt{2}}$$

Power $\propto H(\omega)^2 \Rightarrow P(\omega_0) = \frac{P_{in}}{2}$

\therefore At the cut-off frequency the power is halved

Amplifier

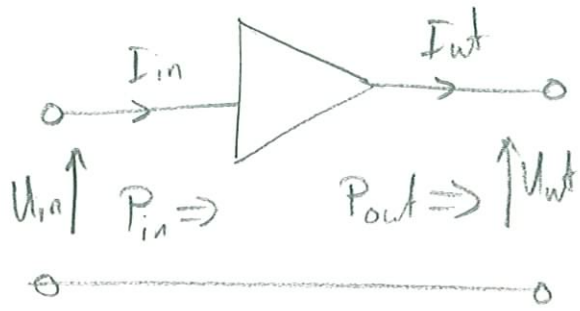

Voltage amplification

$$A_v = \frac{V_{out}}{V_{in}}$$

Current amplification

$$A_i = \frac{I_{out}}{I_{in}}$$

Power amplification

$$A_p = \frac{P_{out}}{P_{in}}$$

Decibel

It is very useful to express amplification and attenuation in dB

$$A_{p\text{dB}} = 10 \log A_p = 10 \log \frac{P_{out}}{P_{in}}$$

$$\text{as } P = V \cdot I = \frac{V^2}{R}$$

$$A_{p\text{dB}} = 10 \log \frac{P_{out}}{P_{in}} = 10 \log \frac{\left(\frac{V_{out}}{R}\right)^2}{\left(\frac{V_{in}}{R}\right)^2} = 10 \log \left(\frac{V_{out}}{V_{in}}\right)^2 = 20 \log \frac{V_{out}}{V_{in}} = A_{v\text{dB}}$$

$$A_{v\text{dB}} = 20 \log \frac{V_{out}}{V_{in}}$$

dB	A_v	A_p
-20 dB	$1/10$	$1/100$
-3 dB	$1/\sqrt{2}$	$1/2$
0 dB	1	1
+3 dB	$\sqrt{2}$	2
+20 dB	10	100

Bode diagram

Absolute value $|H(\omega)|_{dB}$ and phase $\phi = \text{angle}(H(\omega))$ is plotted in two separate graphs with logarithmic frequency axis.


For the RC-filter

$$|H(\omega)| = \frac{1}{\sqrt{1+(\omega RC)^2}} = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_0})^2}} \quad \text{where } \omega_0 = \frac{1}{RC} \text{ cut-off frequency}$$

$$\phi = \text{angle}(H(\omega)) = \arctan\left(\frac{\text{Im}(H(\omega))}{\text{Re}(H(\omega))}\right)$$

$$H(\omega) = \frac{1}{1+j\frac{\omega}{\omega_0}} = \frac{1-j\frac{\omega}{\omega_0}}{\underbrace{(1+j\frac{\omega}{\omega_0})(1-j\frac{\omega}{\omega_0})}_{\text{Real value}}} \Rightarrow \phi = \arctan\left(\frac{-\frac{\omega}{\omega_0}}{1}\right) = \arctan\left(-\frac{\omega}{\omega_0}\right)$$
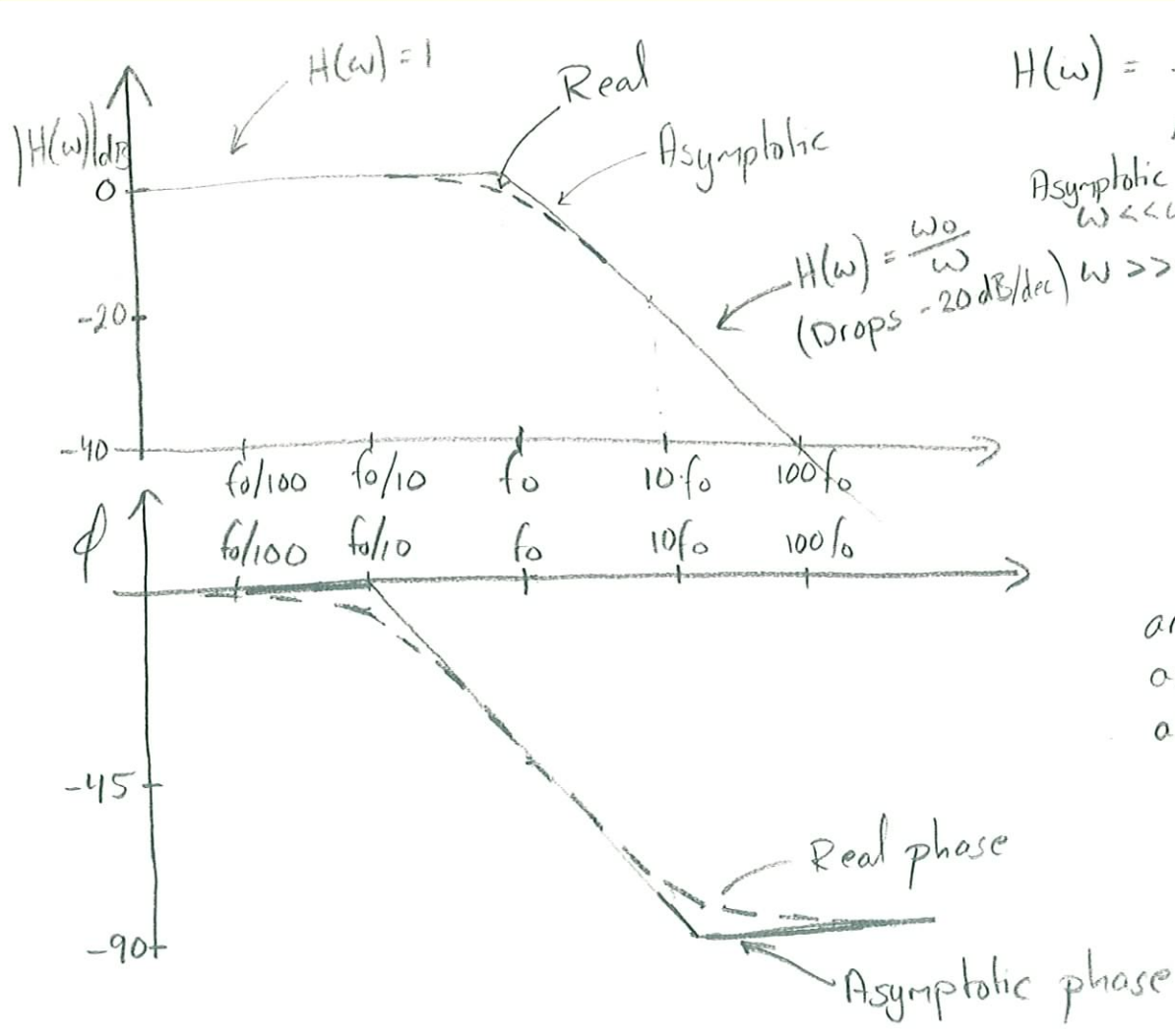
$$\phi = -\arctan\frac{\omega}{\omega_0}$$



$$H(\omega) = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_0})^2}}$$

Asymptotic $\omega \ll \omega_0 \Rightarrow H(\omega) = 1$
 $\omega \gg \omega_0 \Rightarrow H(\omega) = \frac{\omega_0}{\omega}$
 (Drops -20 dB/dec)

$\arctan(0,1) = 5,7^\circ$
 $\arctan(1) = 45^\circ$
 $\arctan(10) = 84,3^\circ$

Complicated expression can be factorized into superexpressions such as

$$(const), j\frac{\omega}{\omega_0}, \frac{1}{j\frac{\omega}{\omega_0}}, 1+j\frac{\omega}{\omega_0}, 1-j\frac{\omega}{\omega_0}$$

The total amplification A_{tot} is then

$$A_{tot} = A_1 \cdot A_2 \cdot A_3$$

or


$$A_{tot\text{dB}} = A_{1\text{dB}} + A_{2\text{dB}} + A_{3\text{dB}} \quad (\text{According to logarithmic laws})$$

and the phase

$$\text{angle}(A_{tot}) = \text{angle}(A_1) + \text{angle}(A_2) + \text{angle}(A_3)$$

lect 1
↓

Ex

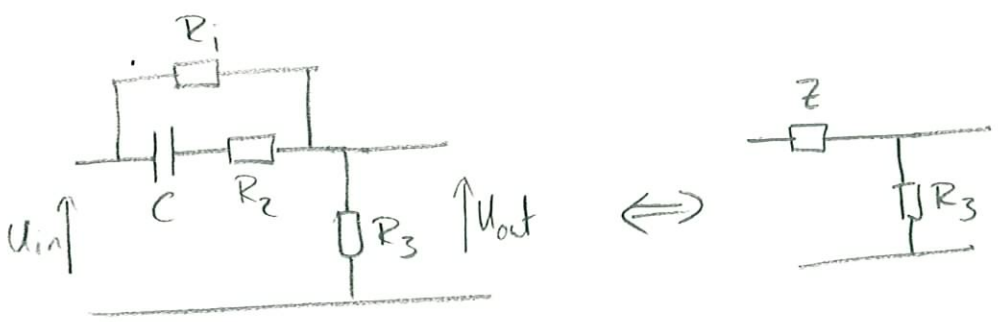

$$Z = R_1 // (R_2 + \frac{1}{j\omega C}) = \frac{R_1 (R_2 + \frac{1}{j\omega C})}{R_1 + R_2 + \frac{1}{j\omega C}} = \frac{R_1 (1 + j\omega R_2 C)}{1 + j\omega (R_1 + R_2) C}$$


$$\frac{U_{out}}{U_{in}} = \frac{R_3}{R_3 + Z} = \frac{R_3}{R_3 + \frac{R_1 (1 + j\omega R_2 C)}{1 + j\omega (R_1 + R_2) C}} = \frac{R_3 (1 + j\omega (R_1 + R_2) C)}{R_3 (1 + j\omega (R_1 + R_2) C) + R_1 (1 + j\omega R_2 C)}$$

$$= \frac{R_3 (1 + j\omega (R_1 + R_2) C)}{R_1 + R_3 + j\omega (R_1 R_2 + R_1 R_3 + R_2 R_3) C} = \text{Break out real part / to leave 1 instead /}$$

$$= \frac{R_3}{R_1 + R_3} \frac{1 + j\omega(R_1 + R_2)C}{1 + j\omega \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 + R_3} C} = K \frac{1 + j \frac{\omega}{\omega_1}}{1 + j \frac{\omega}{\omega_2}} = K \frac{1 + j \frac{f}{f_1}}{1 + j \frac{f}{f_2}}$$



where $K = \frac{R_3}{R_1 + R_3}$
 $f_1 = \frac{1}{2\pi(R_1 + R_2)C}$
 $f_2 = \frac{1}{2\pi(R_1 R_2 + R_1 R_3 + R_2 R_3)C}$

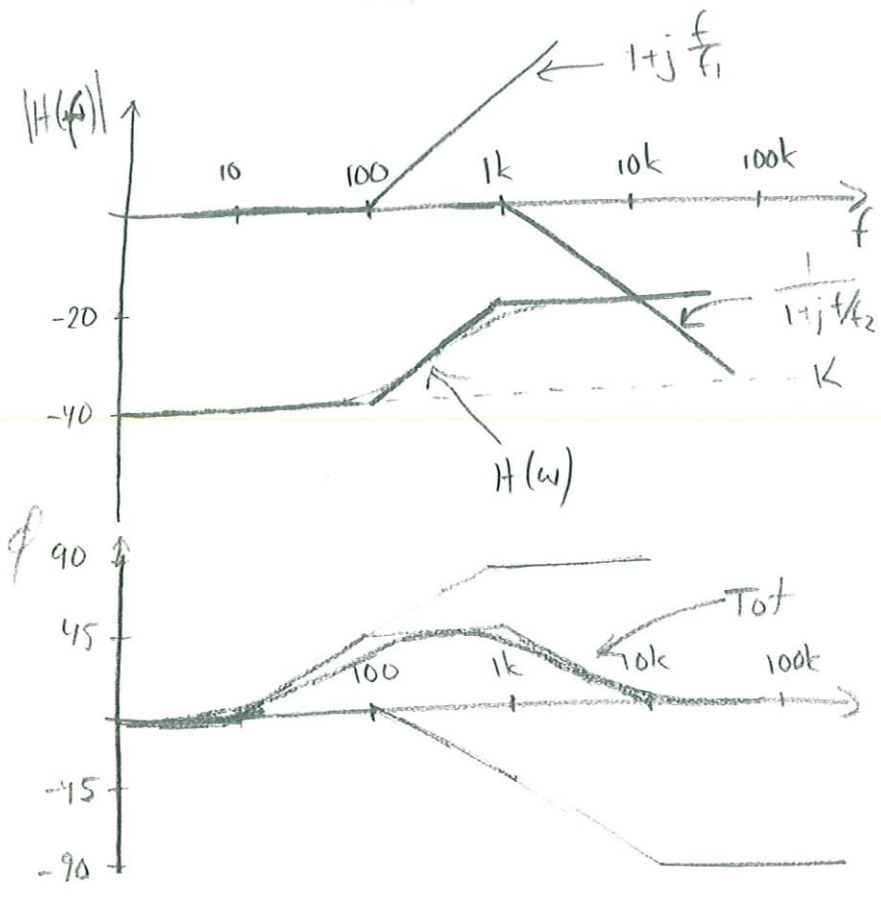Using
 $R_1 = 99k$
 $R_2 = 9.9k$
 $R_3 = 1.0k$
 $C = 14.6nF$
 $K = 0.01$ or $-40dB$
 $f_1 = 100 Hz$
 $f_2 = 1000 Hz$




Pole
 $1 + j \frac{f}{f_p}$

Zero
 $\frac{1}{1 + j \frac{f}{f_z}}$

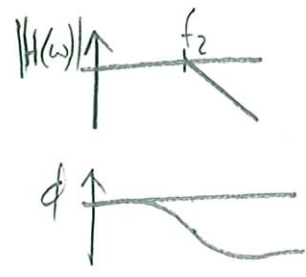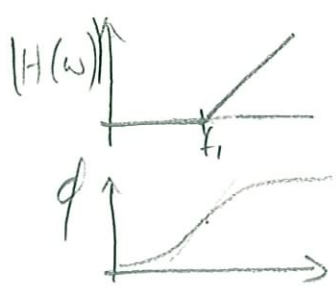


Amplifier model

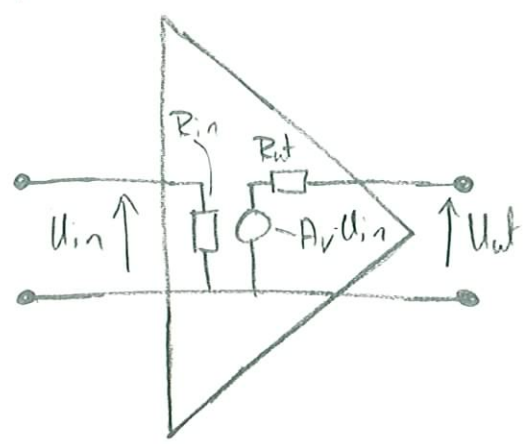

R_{in} - Input resistance
 R_{out} - Output resistance
 A_v - Open loop gain

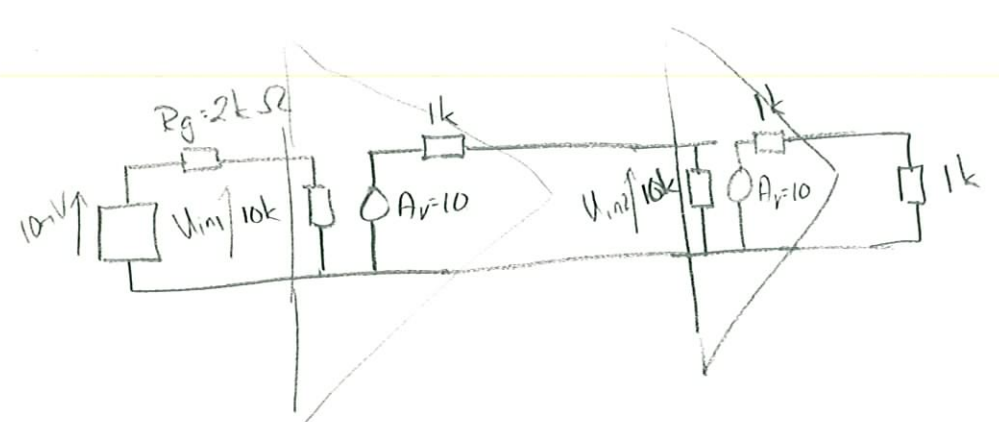Ex 2 Amplifiers with $A_v = 10$ $R_{in} = 10k$ and $R_{out} = 1k$ is cascaded between a generator with $U_{in} = 10mV$ and $R_g = 2k\Omega$ and a load of $1k\Omega$.
 What is the Voltage at the load




$$V_{in1} = V_{in} \frac{10}{10+2} = \frac{V_{in}}{1,2}$$

$$V_{out1} = V_{in2} = 10 \cdot V_{in1} \frac{10}{10+1} = 10 \cdot V_{in1} \cdot \frac{1}{1,1} = \frac{10 \cdot V_{in}}{1,2 \cdot 1,1}$$

$$V_{out2} = V_{in2} \cdot 10 \cdot \frac{1}{1+1} = \frac{10 \cdot V_{in}}{1,1 \cdot 1,2} \cdot 10 \cdot \frac{1}{2} = 37,9 V_{in} = 379 mV$$

Bandwidth

The frequency range for flat gain

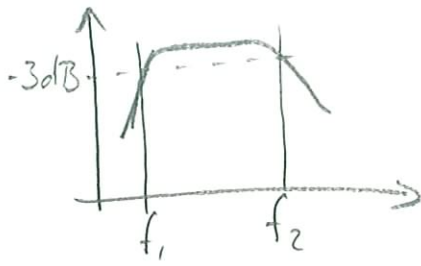


$$BW = f_2 - f_1$$

Distortion

A nonlinear transfer function between U_{in} and U_{out} distorts the signal

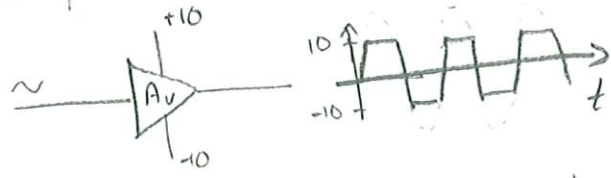- An amplifier that saturates at high voltages



- A diode that conducts only in forward direction

