



Operational Amplifier

OP Amp

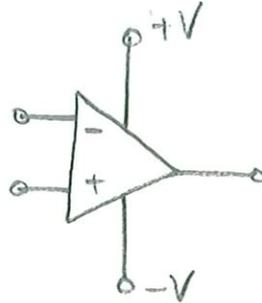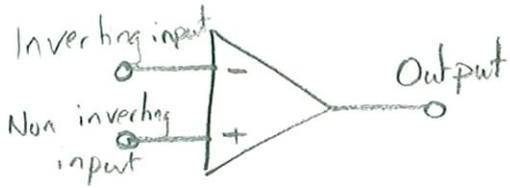2.1

Amplifier with differential input and high gain


- Differential input - Amplifies the Voltage difference



Symbol with supply connection

An operational amplifier is nearly ideal


	Ideal	Practical
A_v	∞	Large
R_{in}	∞	Large
R_{out}	0	Small

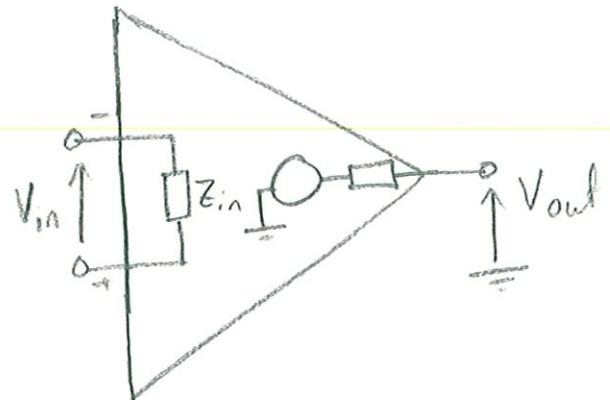


The OP-Amp is used to amplify the difference in voltage between the input

$$V_{out} = (V^+ - V^-) \cdot A_v$$

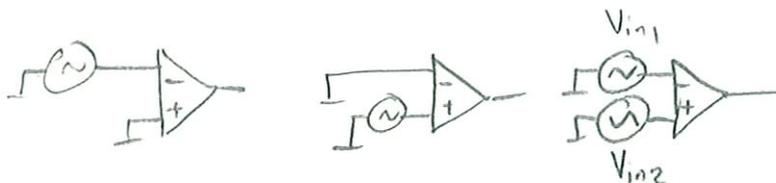⇒ Called differential mode. Either between one input and ground or different signals on both inputs.



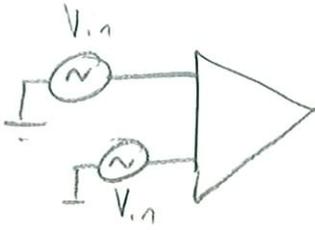Applying the same signal on both input is called "Common mode" and should be as small as possible



Common mode rejection ratio - "CMRR" is the ratio

$$CMRR = \frac{A_{ol}}{A_{cm}} \quad \text{or} \quad = 20 \log \frac{A_{ol}}{A_{cm}}$$

in dB

← A_{ol} - "Open-loop gain"

Ex $A_{ol} = 100 \text{ dB}$
 $A_{cm} = -14 \text{ dB}$

$$100 \text{ dB} \Rightarrow 10^{\frac{100}{20}} = 100\,000$$

$$-14 \text{ dB} \Rightarrow 10^{\frac{-14}{20}} = 0,2$$

$$\underline{CMRR} = \frac{100\,000}{0,2} = \underline{500\,000}$$

$$20 \log 500\,000 = \underline{114 \text{ dB}}$$


Any other way??

$$CMRR = 100 - (-14) = 114 \text{ dB}$$

Basic OP-Amp circuit analysis

- In a circuit the OP-amp drives the output, so that V_{diff} is minimized, read $V_{diff} = 0$

Non inverting amplifier

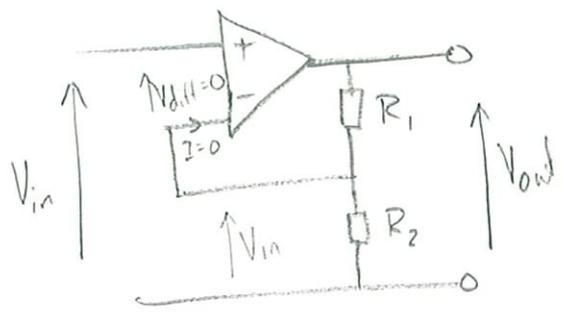


Voltage division

$$V_{in} = V_{out} \frac{R_2}{R_1 + R_2}$$

$$\frac{V_{out}}{V_{in}} = A_V = \frac{R_1 + R_2}{R_2}$$

Inverting amplifier

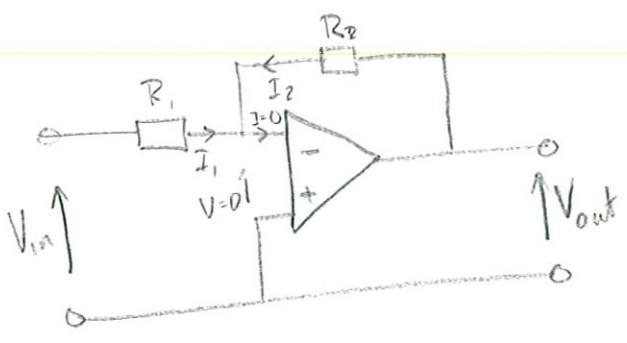


$$I_1 = \frac{V_{in}}{R_1} \quad I_2 = \frac{V_{out}}{R_2} \quad \text{KCL } I_1 = -I_2$$

$$\frac{V_{out}}{R_2} = - \frac{V_{in}}{R_1}$$

$$\frac{V_{out}}{V_{in}} = A_V = - \frac{R_2}{R_1}$$

↑
Inverted or $\phi = 180^\circ$


Voltage follower

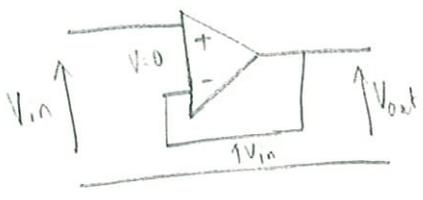

$$V_{out} = V_{in} \quad \frac{V_{out}}{V_{in}} = 1$$

Maximal output swing, $V_{O_{P-P}}$

2.4

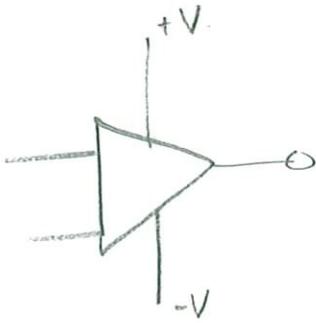

⇒ the OP-amp is normally fed with a supply voltage that limits the output swing.

⇒ In practice the output is even less than this.

In a KA741 fed with $\pm 15V$ the output is limited to $V_{O_{P-P}} = \pm 13V$

Some OP-Amps labeled Rail-to-Rail can deliver all the way to the supply voltage.

Input offset voltage

Ideally $V_{out} = 0$ when $V_{in} = 0$ but in practice due to mismatch


$V_{out} = 0$ when a small voltage difference occurs at the input

V_{io} which is typically in the range 2mV or less.

KA 741	
typ	max
V_{IO}	2mV 6mV

Input bias current, I_{BIAS}

In reality $I_{in} \neq 0$

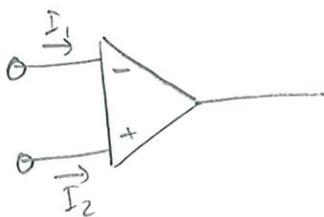

I_{BIAS} is the mean value of the two small input currents

$$I_{BIAS} = \frac{I_1 + I_2}{2}$$

As $I_1 \neq I_2$ the difference is called

Input offset current

$$I_{os} = |I_1 - I_2|$$

KA 741		
	typ	max
I_{BIAS}	80nA	500nA
I_{os}	20nA	200nA


Input and Output resistances

KA 741
min typ
 R_I 0.3M Ω 2M Ω

R_{out} is very low but the output current is often limited to protect the device from destruction

Frequency response

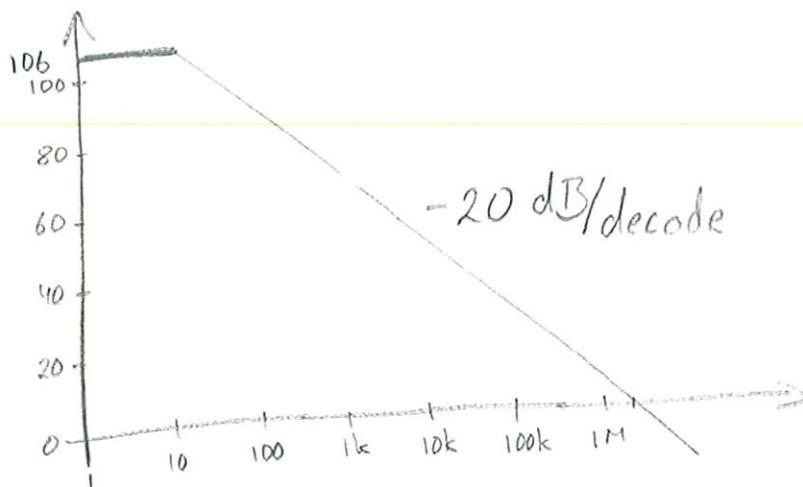
Open-loop gain A_{ol} decreases with frequency




\therefore At high frequencies the gain is less.

The output rate of change is limited by the "Slew rate"
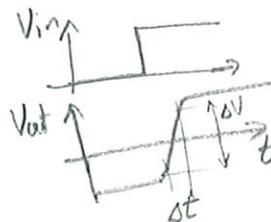
$$\text{Slew rate} = \frac{\Delta V_{out}}{\Delta t}$$



Ex | Calculate the cut-off frequency due to slew rate.

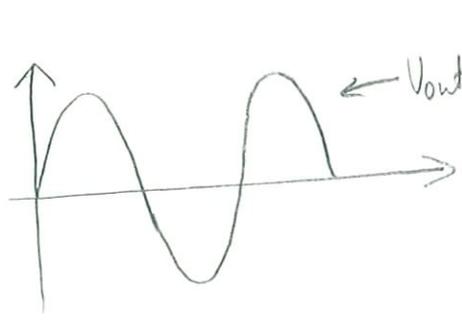

The derivative V_{out}' is the rate of change

$$V_{out}' = \frac{dV_{out}}{dt} = \hat{U} \cdot \omega \cos(\omega t)$$

$$\left. \frac{dV_{out}}{dt} \right|_{max} = \text{slew rate}$$


$$SR = \hat{U} \cdot \omega = \hat{U} \cdot 2\pi f$$

$$f_{max} = \frac{SR}{2\pi \hat{U}}$$

∴ At large signals the Bandwidth is less

Negative feed-back

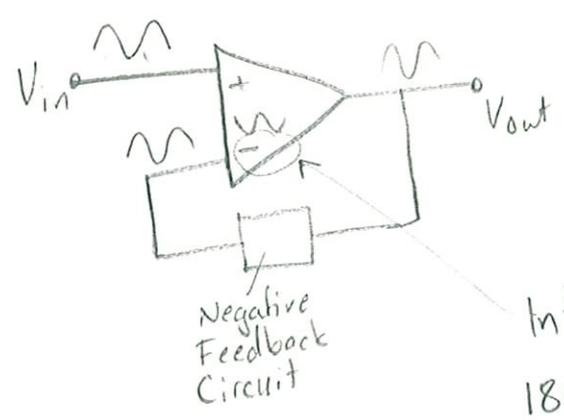- A portion of the output is returned and subtracted from the input




Internal inversion makes V_F 180° out of phase compared to V_{in}

Why use negative feedback

- Gain is reduced to desired value for stable operation
- The bandwidth is significantly increased
- The linearity is significantly improved
- Input resistance can be increased or reduced to some desired value
- Output resistance can be reduced to a desired value.

OP-Amp configurations

- Non inverting amplifier

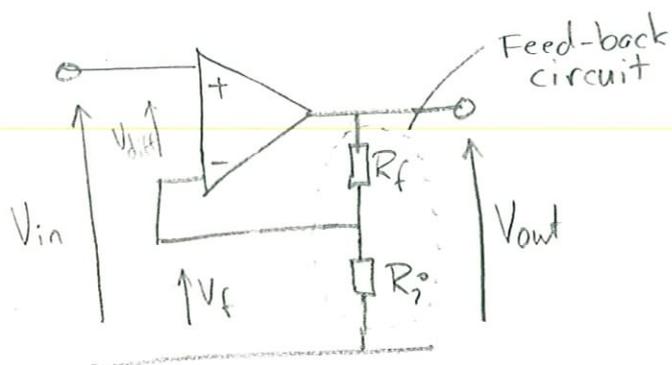

$$V_{out} = A_{ol}(V_{in} - V_f)$$

The feedback factor

$$B = \frac{R_i}{R_i + R_f} \quad \left(\text{Portion of signal that are fed back} \right)$$

$$V_{out} = A_{ol}(V_{in} - V_{out} \cdot B)$$

$$V_{out} = A_{ol} \cdot V_{in} - V_{out} A_{ol} \cdot B$$

$$V_{out}(1 + A_{ol} \cdot B) = A_{ol} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_{ol}}{1 + A_{ol} \cdot B}$$

$A_{ol} \cdot B$ is often $\gg 1$

$$\frac{V_{out}}{V_{in}} \approx \frac{A_{ol}}{A_{ol} \cdot B} = \frac{1}{B}$$


$$\frac{V_{out}}{V_{in}} = A_{cl} \approx \frac{1}{B} = \frac{R_i + R_f}{R_i}$$

↑
closed loop

∴ Independent on A_{ol} as long as $A_{ol} \cdot B \gg 1$

Effect on impedances

Input Impedance

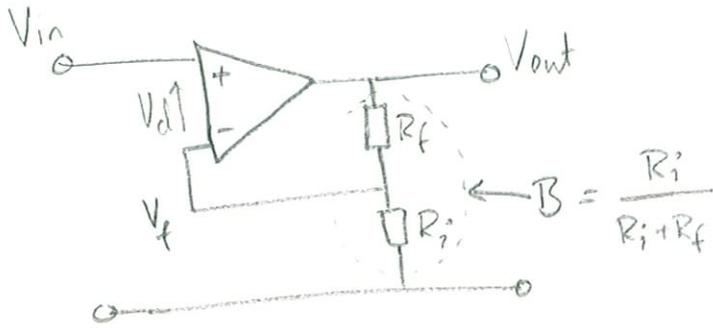

$$V_f = B \cdot V_{out} \Rightarrow V_{in} = V_d + B \cdot V_{out} = V_d + B \underbrace{V_d \cdot A_{ol}}_{= V_d \cdot A_{ol}} = V_d (1 + B A_{ol}) = V_d \underbrace{(1 + B A_{ol})}_{= I_{in} Z_{in}}$$

Open loop Z_{in}


$$V_{in} = (1 + B \cdot A_{ol}) I_{in} \cdot Z_{in} \quad \frac{V_{in}}{I_{in}} = (1 + B \cdot A_{ol}) \cdot Z_{in}$$

$Z_{in(NI)}$

$$Z_{in(NI)} = (1 + B \cdot A_{ol}) \cdot Z_{in} \quad \because Z_{in(NI)} \gg Z_{in}$$

Let 3

Output impedance

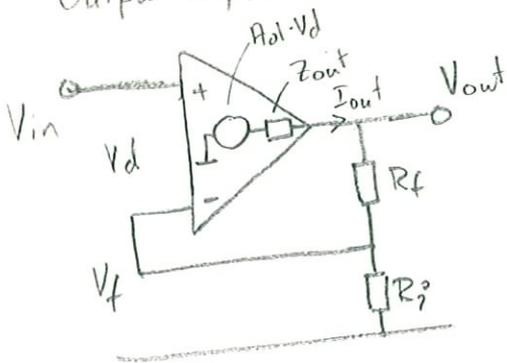

$$V_{out} = A_{ol} \cdot V_d - \underbrace{I_{out} \cdot Z_{out}}_{\ll A_{ol} \cdot V_d} \approx A_{ol} (V_{in} - V_f) = A_{ol} (V_{in} - B \cdot V_{out})$$

$$V_{out} \approx A_{ol} \cdot V_{in} - A_{ol} \cdot B \cdot V_{out}$$

$$V_{out} (1 + A_{ol} \cdot B) \approx A_{ol} \cdot V_{in}$$

$I_{out} \cdot Z_{out(NI)}$

$$I_{out} \cdot Z_{out(NI)} (1 + A_{ol} \cdot B) \approx A_{ol} \cdot V_{in}$$

$$\frac{A_{ol} \cdot V_{in} \cdot \underbrace{V_{out(ol)}}_{V_{out(ol)}}}{I_{out}} = (1 + A_{ol} \cdot B) Z_{out(NI)}$$

Z_{out}

$$\Rightarrow Z_{out(NI)} = \frac{Z_{out}}{1 + A_{ol} \cdot B}$$


$\because Z_{out}$ is reduced with feedback

A Voltage follower is a non-inverting amplifier with $\beta=1$

$$\Rightarrow Z_{in(VF)} = (1 + A_{ol}) Z_{in}$$

$$Z_{out(VF)} = \frac{Z_{out}}{1 + A_{ol}}$$


For an inverting amplifier

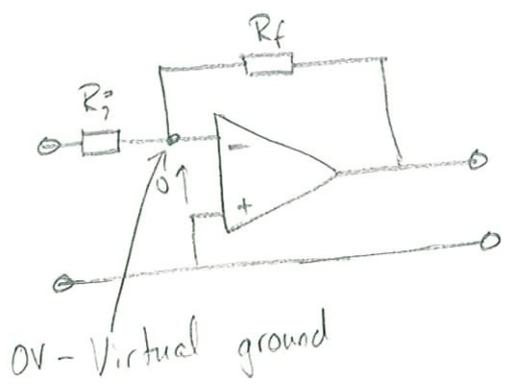

$$Z_{out(I)} = \frac{Z_{out}}{1 + A_{ol} B}$$


Bias current compensation

Inverting

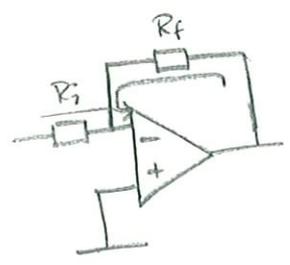


$$V_{oo} = I_{io} \cdot R_f$$

Non inverting

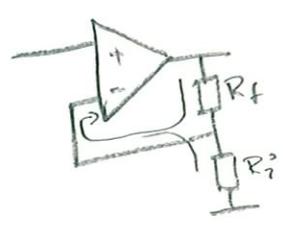




$$V_{oo} = I_{io} \cdot R_f$$

Voltage follower

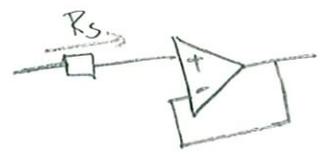


$$V_{oo} = I_{io} \cdot R_s$$

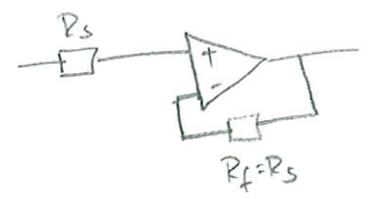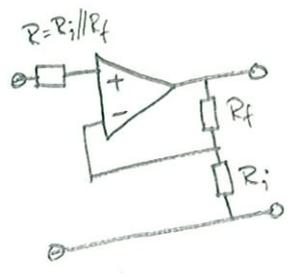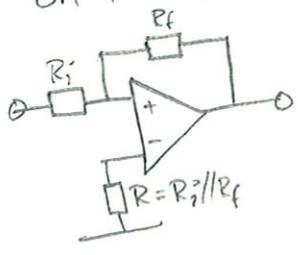Bias current compensation is achieved by adding a resistor on the other input opposing the first one




Input offset voltage compensation

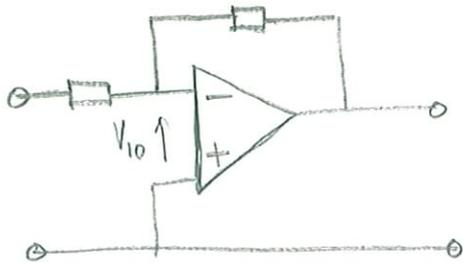


V_{10} is generally amplified by A_{cl}

$$V_{00} = V_{10} \cdot A_{cl}$$

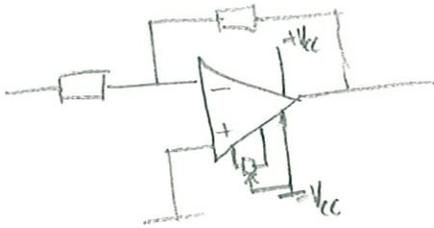OP-Amps have often designated pins for compensation
for instance $\mu A741$



Closed loop frequency response

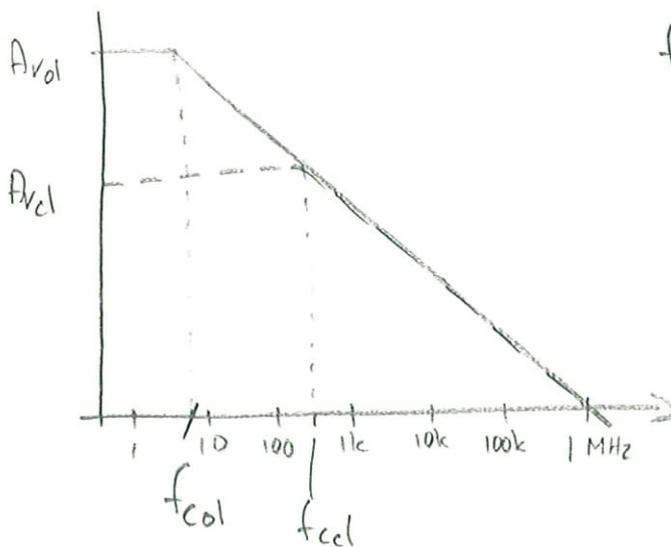


$$f_{ccl} = f_{col} (1 + B \cdot A_{ol})$$

∴ High gain \rightarrow small bandwidth
low gain \rightarrow large bandwidth

Gain Bandwidth product

$$A_{cl} f_{ccl} = A_{ol} \cdot f_{col} = f_T \quad (\text{The frequency where } A_{ol} = 0 \text{ dB})$$

Stability

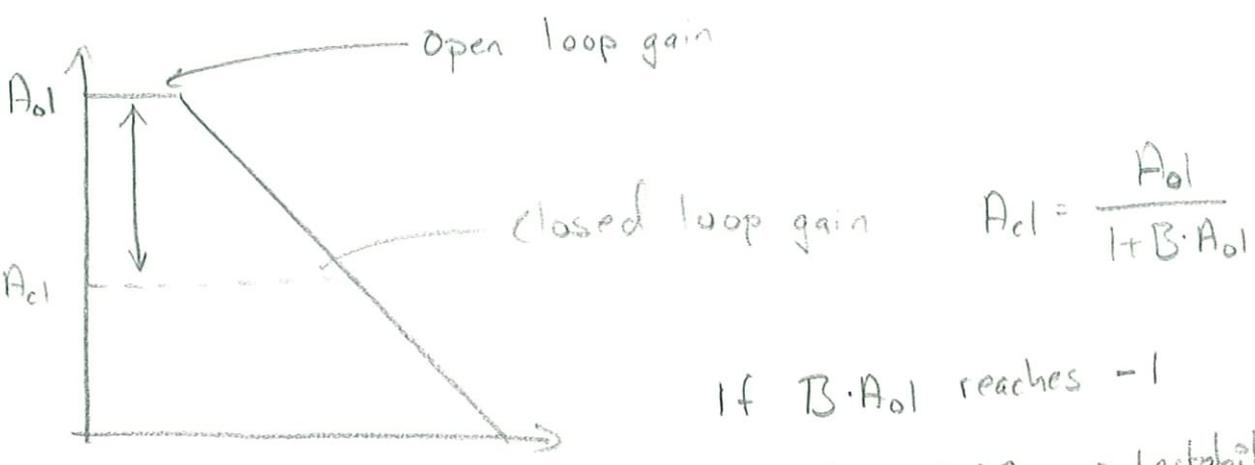


If $B \cdot A_{ol}$ reaches -1
 $\Rightarrow A_{cl} \rightarrow \infty \rightarrow$ Instability

$B \cdot A_{ol}$ is called loop gain and is the key for study of instability

Stability criteria


$$A_{ol} \cdot B < -1 \text{ or } > 1 \angle -180^\circ$$

Nyquist diagram

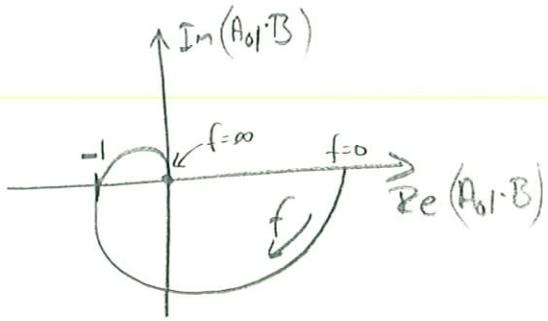


For stable operation some margin is required

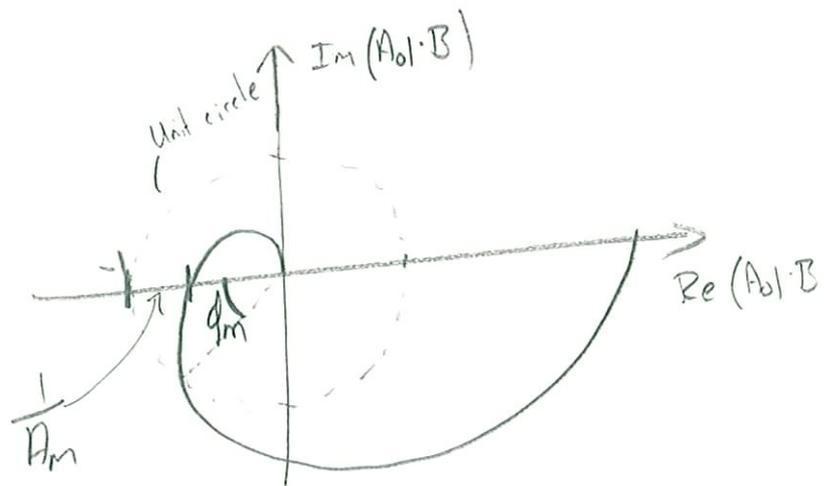Either Amplitude margin, A_m or Phase margin, ϕ_m




Rule of thumb : $\phi_m > 45^\circ$ and $A_m > 2$ (6dB) for stable operation
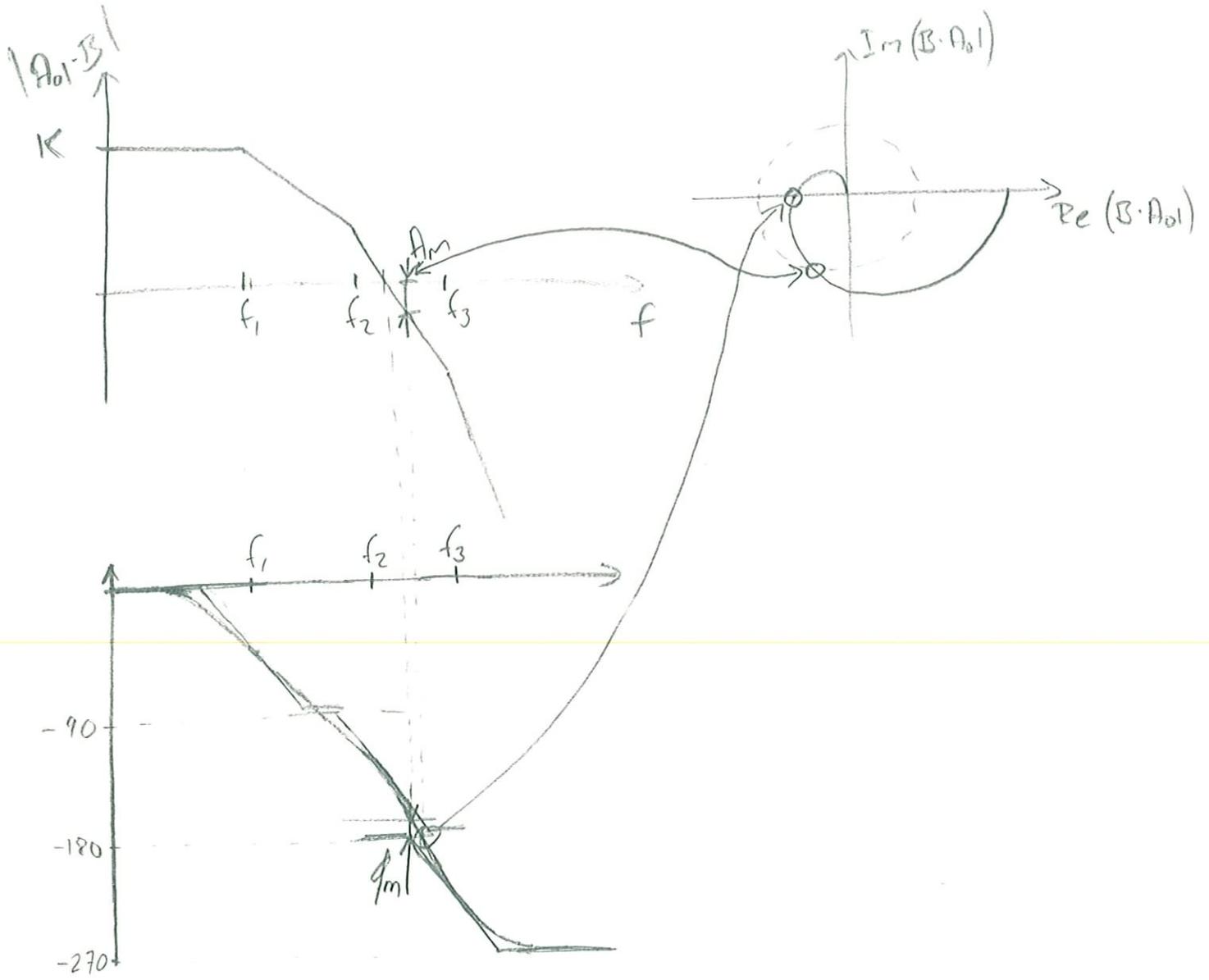
$$A_{ol} \cdot B = \frac{K}{(1+j\frac{f}{f_1})(1+j\frac{f}{f_2})(1+j\frac{f}{f_3})}$$



Ex | In what ranges of resistive feed-back is the following amplifier stable, nearly stable and unstable

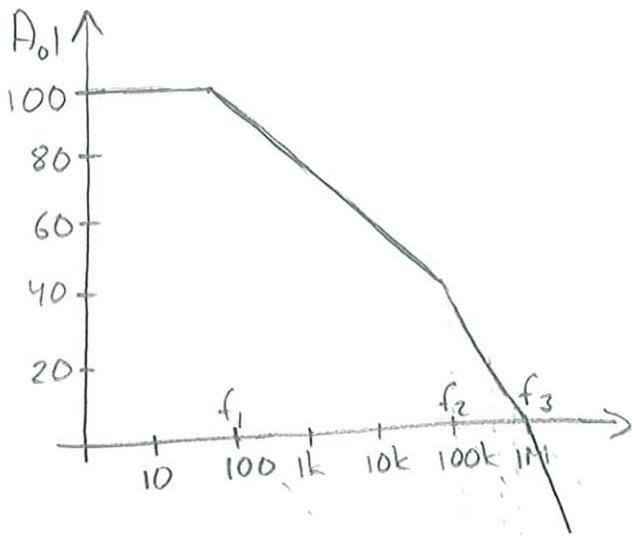
$$A_{ol} = \frac{100\,000}{(1+j\frac{f}{100})(1+j\frac{f}{100k})(1+j\frac{f}{1M})}$$



Phase margin ϕ_m

Unstable < 0
 Nearly stable $0 - 45^\circ$
 Stable $> 45^\circ$

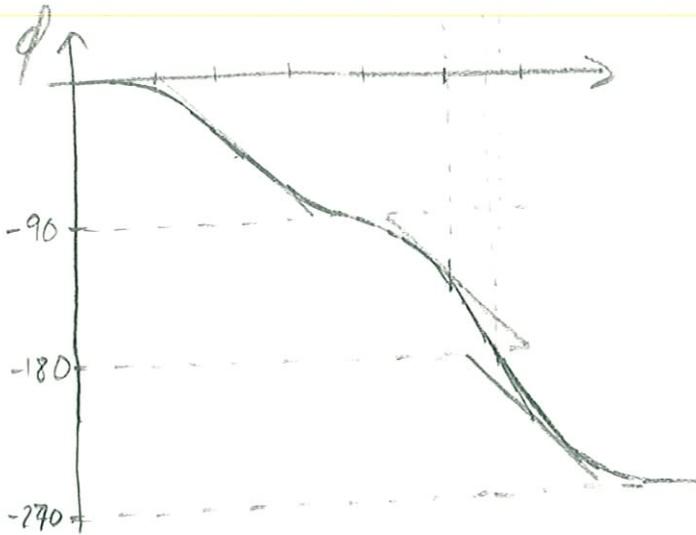$\phi = -180^\circ \sim f = 300\text{ kHz}, A_{ol} = 20\text{ dB}$
 $\phi = -135^\circ \sim f = 100\text{ kHz}, A_{ol} = 40\text{ dB}$



for $\beta = 0$ (No feed-back)
 $A_{ol} \cdot \beta < 0\text{ dB} \Rightarrow$ stable

for $\beta = 1$ (Unit gain)
 $A_{ol} \cdot \beta > 0$ where $\phi = -180^\circ \Rightarrow$ Unstable



With $\beta = -20\text{ dB}$ or 0.1
 $A_{ol} \cdot \beta = 0$ where $\phi = -180^\circ$

With $\beta = -40\text{ dB}$ or 0.01
 $A_{ol} \cdot \beta = 0$ where $\phi = -135^\circ$

	β	A_v
Stable	$0 \rightarrow 0.01$	$A_{ol} - 40\text{ dB}$
Nearly stable	$0.01 \rightarrow 0.1$	$40 - 20\text{ dB}$
Unstable	$0.1 \rightarrow 1$	$20 - 0\text{ dB}$

Driving capacitive loads can give stability problems for otherwise stable circuits

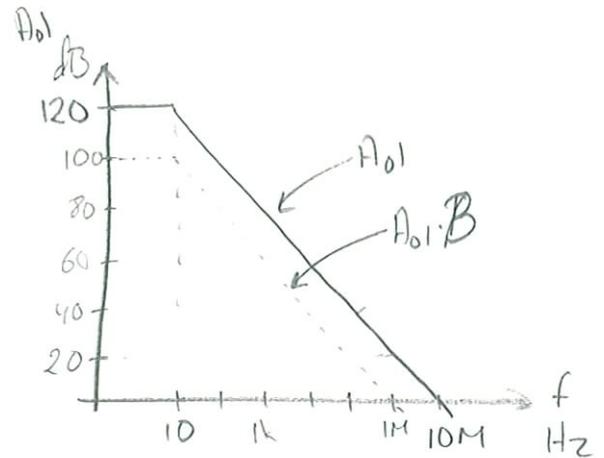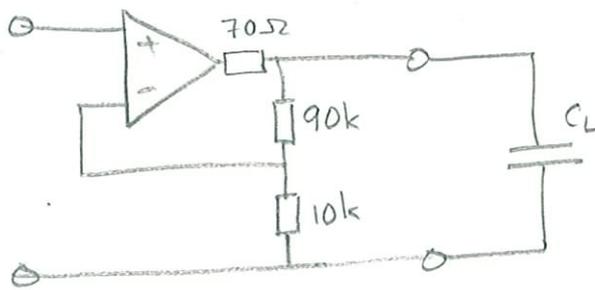Ex1 calculate how long wire with $C = 100 \text{ pF/m}$ the following amplifier can drive.



$$A_v = \frac{90 + 10}{10} = 10 \text{ times or } 20 \text{ dB}$$

$$B = \frac{10\text{k}}{10\text{k} + 90\text{k}} = 0,1$$

With $B = 10$, $A_{ol} \cdot B = 0 \text{ dB}$ @ 1 MHz


The pole @ 10 Hz gives -90° phase > 100 Hz

Placing the 2nd pole at 1 MHz gives $\phi = 90 - 45 = -135^\circ$ or

$$\phi_m = 45^\circ @ 1 \text{ MHz}$$

$$f_c = \frac{1}{2\pi RC} \Rightarrow C_{\text{max}} = \frac{1}{2\pi R f_c} = \frac{1}{2\pi \cdot 70 \cdot 1 \cdot 10^6} = 2,3 \text{ nF}$$

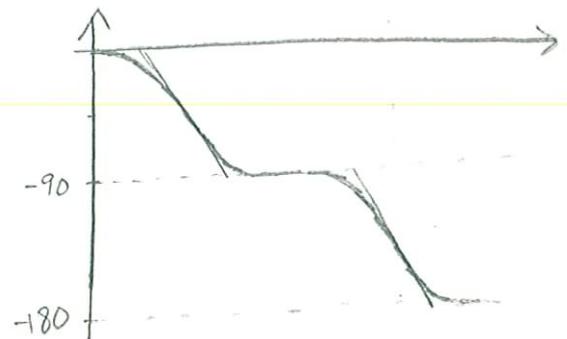
$$\text{wire length } l = \frac{C_{\text{max}}}{C_{\text{wire}}} = \frac{2,3 \text{ nF}}{100 \text{ pF/m}} = 23 \text{ m}$$



OP-amp compensation


Most sold OP-amps are internally compensated to give stable operation in most cases.

OP-amp block diagram

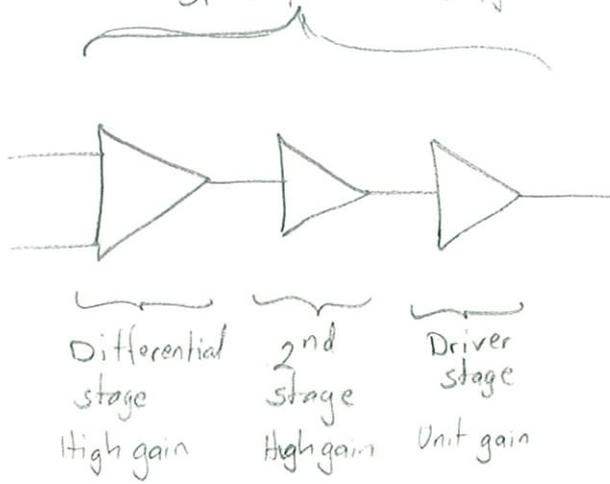


Internal compensation is often achieved by "Dominant pole compensation" using a "Miller capacitor" on the 2nd stage

Miller Capacitor

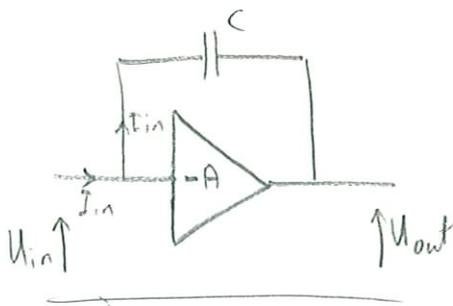


$$\left. \begin{aligned} U_{in} - U_{out} &= I_{in} \cdot \frac{1}{j\omega C} \\ U_{out} &= U_{in} \cdot (-A) \end{aligned} \right\} U_{in}(1+A) = \frac{I_{in}}{j\omega C}$$
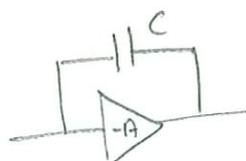
$$Z_{in} = \frac{U_{in}}{I_{in}} = \frac{1}{j\omega C(1+A)}$$




\Rightarrow

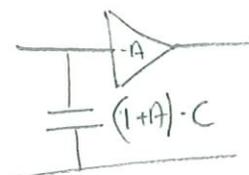

Dominant pole compensation

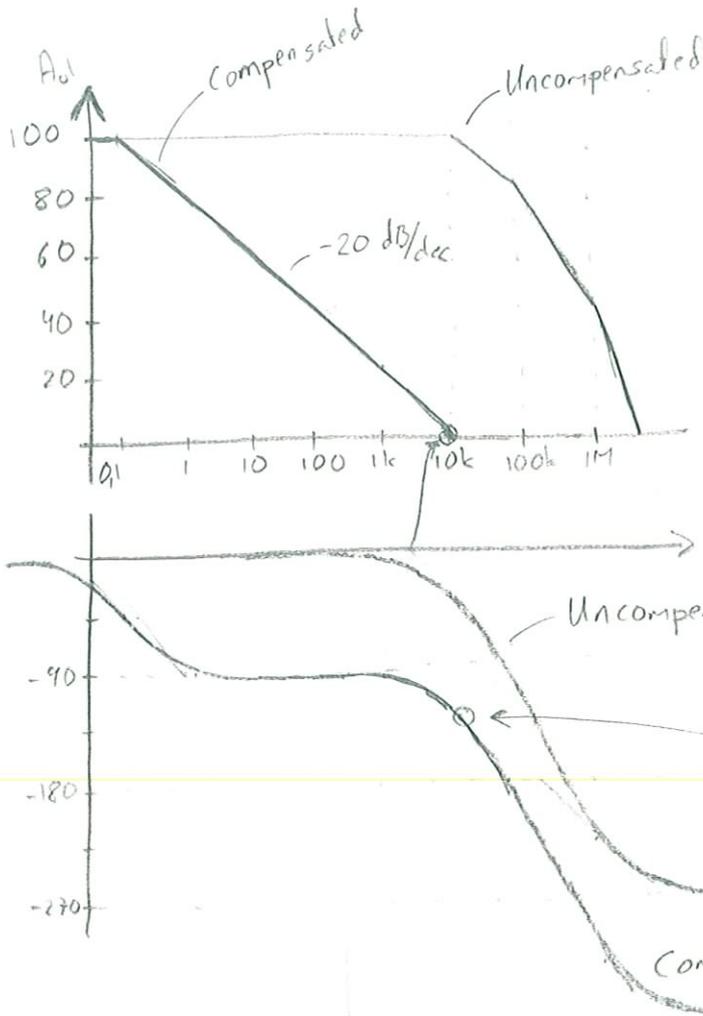Assume $A_{ol} = \frac{100\,000}{(1+j\frac{f}{10k})(1+j\frac{f}{100k})(1+j\frac{f}{1M})}$



For unit gain ($B=1$)

$B \cdot A_{ol} > 1$ where $\phi_m = 45^\circ$

\Rightarrow Unstable

Compensate the OP-amp with a dominant pole to be stable for unit gain.

\Rightarrow A new pole at low frequencies will give additional -90° in phase shift
 $\Rightarrow \phi = -135^\circ$ ($\phi_m = 45^\circ$) the occur at the first pole for the amplifier, 10kHz

\Rightarrow The gain must be reduced to 0dB at 10kHz for stable operation

$\Rightarrow -20$ dB/decade slope gives $f_o = 0.1$ Hz


\Rightarrow Stable operation down to unit gain

\Rightarrow Much reduced possible bandwidth.

Gain compensation

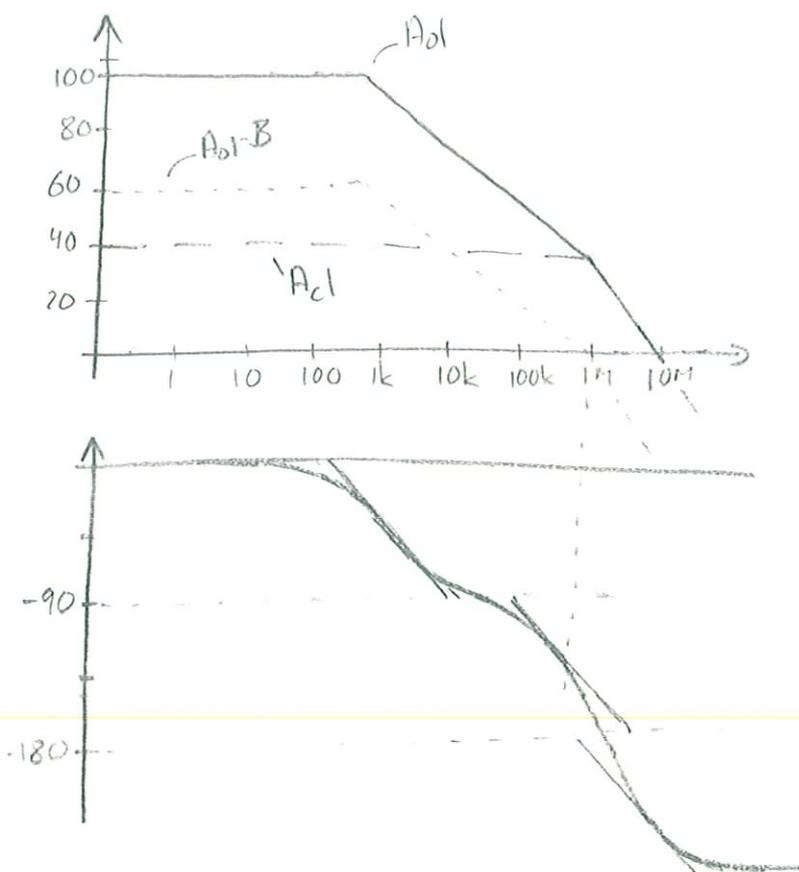2.17

Assume $A_{ol} = \frac{100\,000}{(1+j\frac{f}{1k})(1+j\frac{f}{1M})(1+j\frac{f}{10M})}$



$\phi = -135^\circ$ or $\phi_m = 45^\circ$ @ 1 MHz
where $A_{ol} = 40$ dB

For $B = -40$ dB or 0.01

$B \cdot A_{ol} = 0$ dB where $\phi_m = 45^\circ$

$A_{cl} = \frac{1}{B} = 100$ or 40 dB

Bandwidth $BW = 1$ MHz



⇒ As long as the application can stand the higher gain gain compensation is the best method used.

⇒ Uncompensated versions of normally internally compensated ones are available for tailored external compensation.

Lead compensation

⇒ A phase advancing filter is used to improve f_m at high freq.

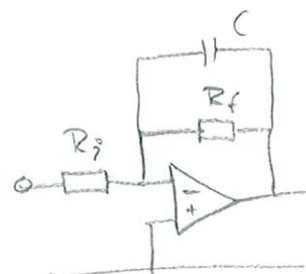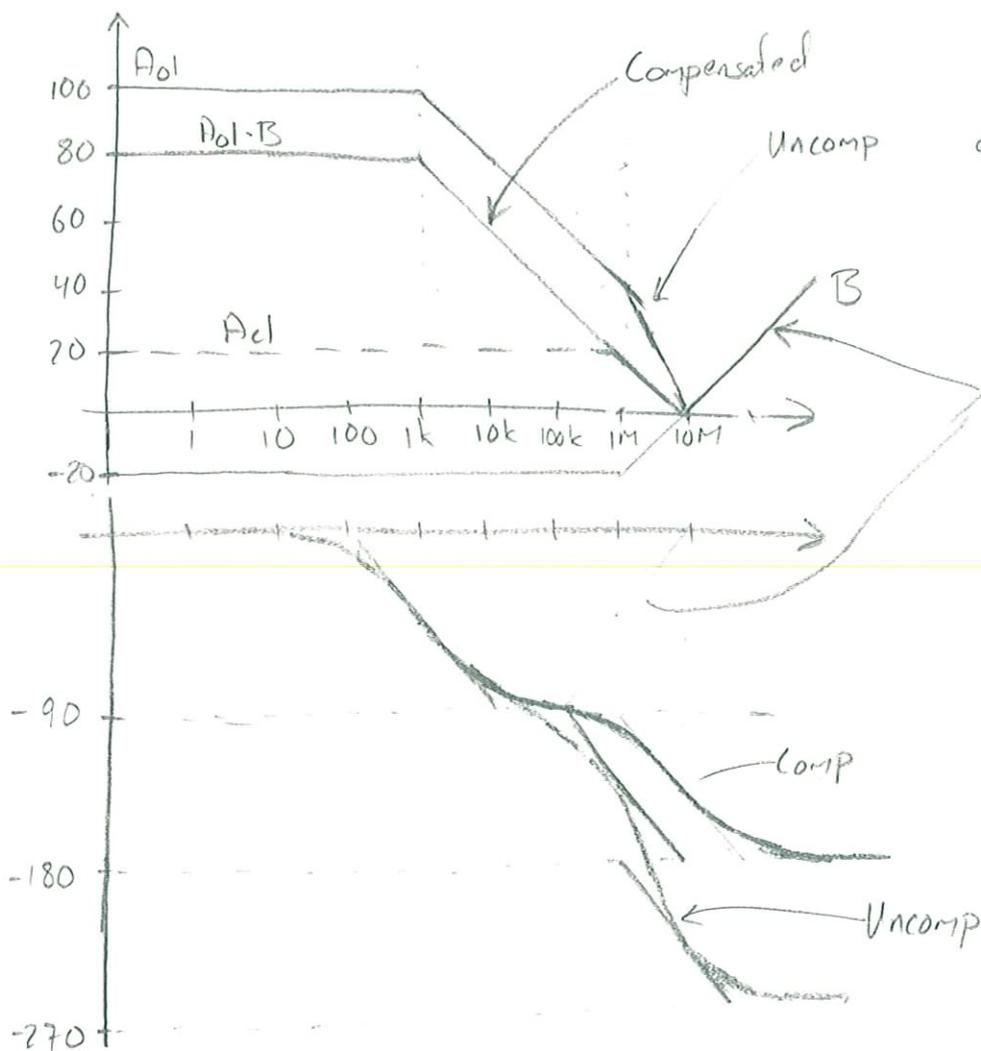Assume $A_{ol} = \frac{100\ 000}{(1+j\frac{f}{1k})(1+j\frac{f}{1M})(1+j\frac{f}{10M})}$



Phase advancing filter

$$A_v = \frac{R_f // C}{R_1} = \frac{R_f \frac{1}{j\omega C}}{R_1 (R_f + \frac{1}{j\omega C})}$$

$$= \frac{R_f}{R_1 (1 + j\omega R_f C)} = \frac{1}{B}$$

$$B = \frac{R_1}{R_f} (1 + j\omega R_f C)$$

Ex1 Assume 10x amplification is desired ($B=0,1$ or -20 dB)

Let $R_1 = 10\text{ k}\Omega$ and $R_f = 100\text{ k}\Omega$

∴ 20 dB gain with $BW = 1\text{ MHz}$