

Discrete semiconductor devices

3.1

⇒ Rectifier (Diode)


- LEDs
- Zener diodes
- Photodiode

⇒ Transistors

- Bipolar transistors
- MOSFETs



Diodes

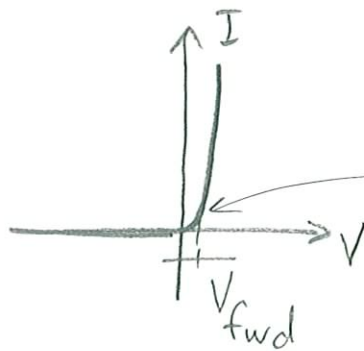2 terminal device that conduct current in one direction and an isolator in the reverse direction




Exponential increased current

V_{fwd} typically 0,6-0,7 V

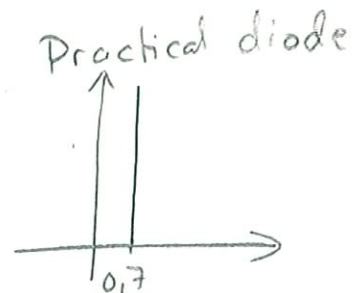
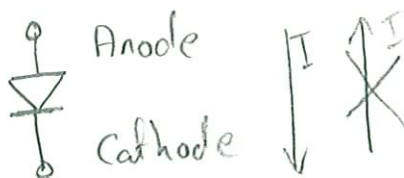


Ex

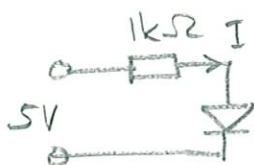



$V > 0,7V \rightarrow$ Diode conducts $\rightarrow V_D = 0,7V$
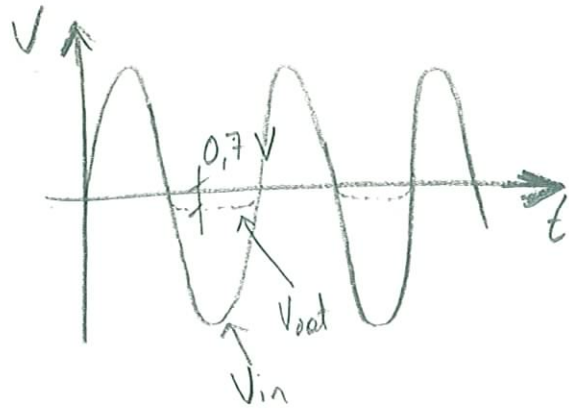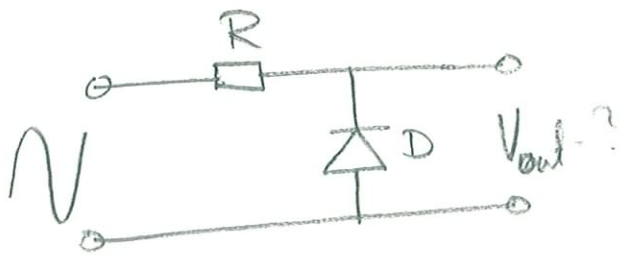
$$I = \frac{V_R}{R} = \frac{5 - 0,7}{1k} = \frac{4,3}{1k} = 4,3 \text{ mA}$$





Zener diode

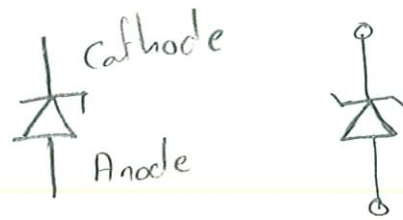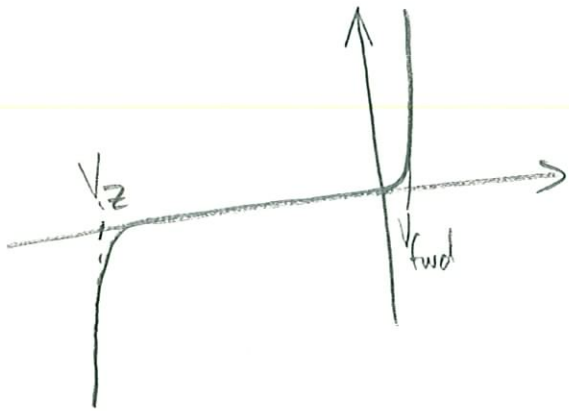Diode that also starts to conduct at a specific reverse voltage, V_Z .



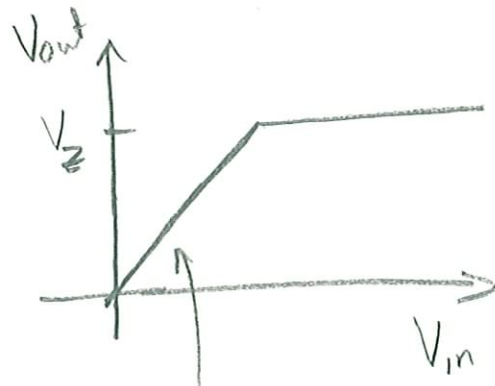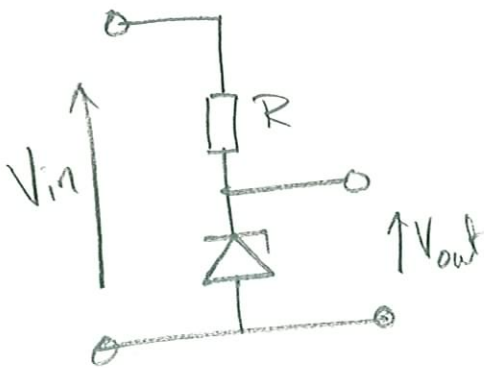Zener diodes are often used to give a constant voltage



$V_{in} < V_Z \rightarrow$ Diode isolator. $\rightarrow I = 0 \rightarrow V_Z = 0$
 $\Rightarrow V_{out} = V_{in}$
 $V_{in} > V_Z \rightarrow$ Diode conducts with
 $V_D = V_Z = V_{out}$

Light emitting diode (LED)



Diode that emits light when current flows in forward direction

V_F depends on what color the specific diode shines with. on is approximately

$$V_{Fwd} \approx h\nu = h \frac{c_0}{\lambda}$$

↑
Planck const in eV


Ex Red LED with $\lambda = 660\text{nm}$

$$V_{Fwd} = h \cdot \frac{c_0}{\lambda} = 4,14 \cdot 10^{-15} \frac{3 \cdot 10^8}{660 \cdot 10^{-9}} = 1,9 \text{ V}$$

Photodiode



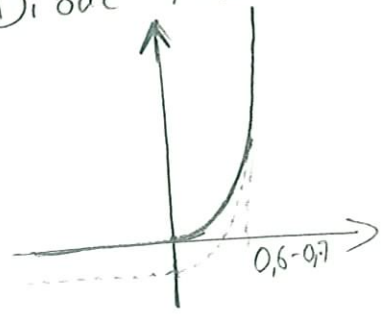Diode that reacts on incoming light
Leakage current in reverse direction increases proportional to the incoming light.



Can be used both at zero volt or any reverse bias.




Transistors

3.4

- Electronic 'valve'
 - The electron current is controlled with either a voltage or a current
 - Millions of transistors is connected in integrated circuits
 - Discrete transistors is often used in power applications
 - Driving high currents
 - Blocking high voltages
-

MOSFET

A MOSFET is voltage controlled device

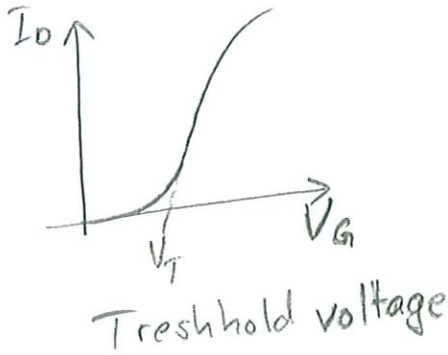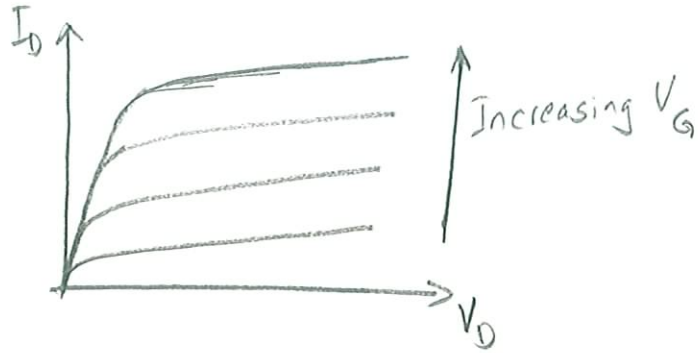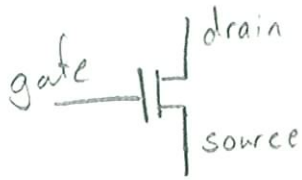


⇒ Gate isolated
 $I_G = 0$


Often used as a switch in switched power applications.

$$V_G = 0 \Rightarrow I = 0$$
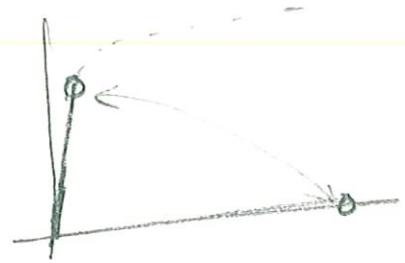
$$V_G > V_T \Rightarrow I \approx \frac{V_D}{R_{DS(on)}}$$




Ex1 Switching analog signal

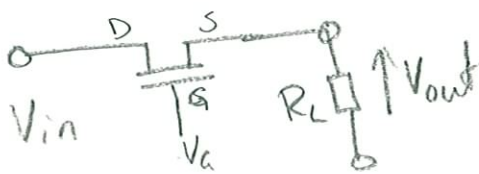

$$V_G = 0 \Rightarrow V_{out} = 0$$


$$V_G > V_{th} \Rightarrow V_{out} = V_{in} \quad (\text{If } R_L \gg R_{DS(on)})$$

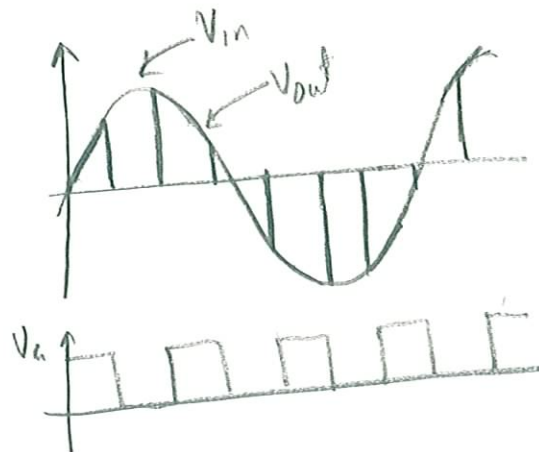Notice that the source voltage must be low enough so that $V_{GS} > V_{TH}$



Bipolar transistors

- Current controlled

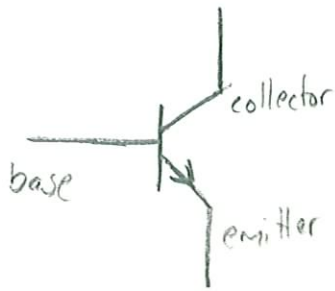


NPN

- A small base-emitter current I_b controls a larger collector-emitter current I_c

$$I_c = \beta \cdot I_b \text{ where } \beta \text{ is the current amplification factor.}$$


β is typically 10-500

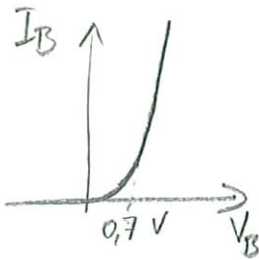The base-emitter junction is a p-n diode junction



The collector current saturates shortly to

$$I_c = \beta \cdot I_b$$

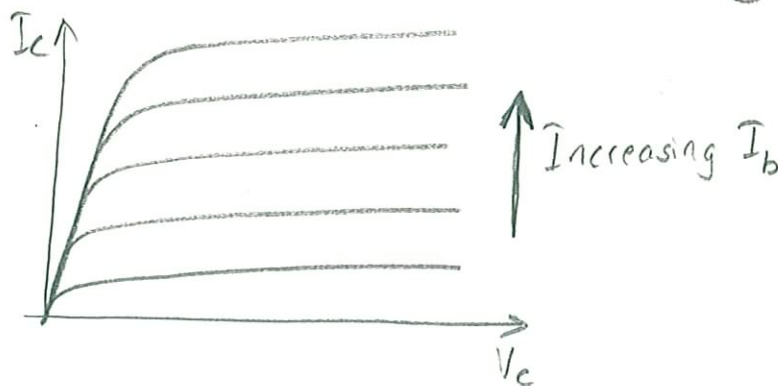

A PNP transistor have opposite characteristics




Ex Driving a LED from a digital output

$$I_{\text{omax}} = 1 \text{ mA}, V_{\text{cc}} = 5 \text{ V}$$

$$V_{\text{out}} = 5 \text{ V}$$

LED $V_F = 1,9 \text{ V}$
 $I_{F_{\text{max}}} = 30 \text{ mA}$

Transistor $\beta_{\text{min}} = 50$

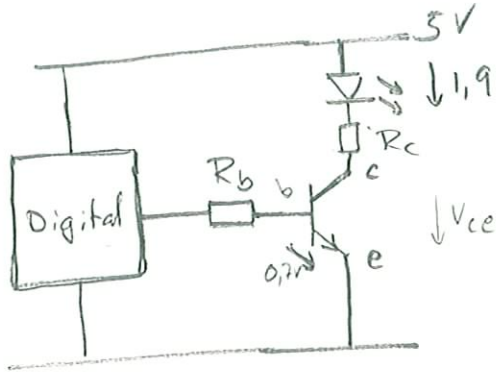

Design

$$I_{F_{\text{max}}} = 30 \text{ mA} \rightarrow I_{C_{\text{max}}} = 30 \text{ mA}$$

In saturation V_{ce} is low typically $0,2 \text{ V}$ and can be neglected

$$R_c = \frac{V_{R_c}}{I_c} = \frac{5 - 1,9}{30 \text{ mA}} = 103 \quad \text{select } \underline{\underline{110 \Omega}}$$

β is at least 50 times

$$\Rightarrow I_b = \frac{I_c}{100} = \frac{30 \text{ mA}}{100} = 0,3 \text{ mA}$$

$$R_b = \frac{V_{R_b}}{I_b} = \frac{5 - 0,7}{0,3 \text{ mA}} = 7,2 \text{ k}\Omega \quad \text{select } \underline{\underline{6,8 \text{ k}\Omega}}$$