
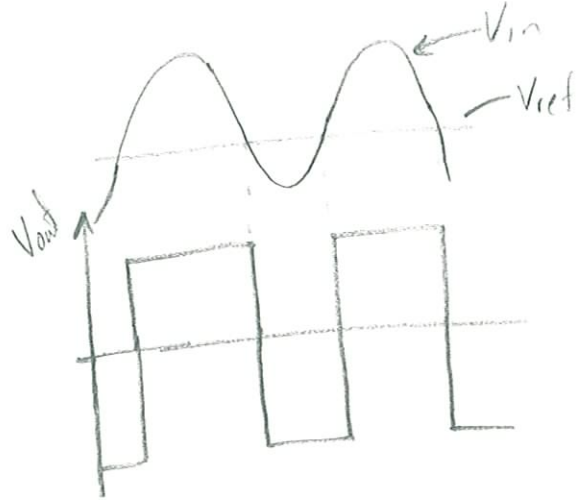


More OP-amp circuits



Comparator

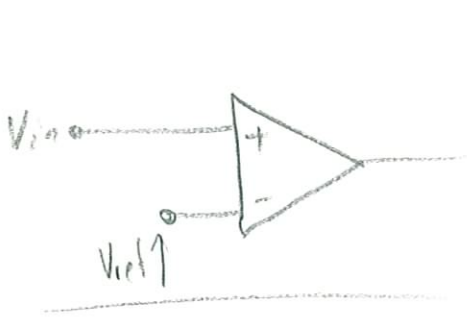- Comparing two signals and toggle between the power feeding levels depending which is greatest




The voltage reference can either be

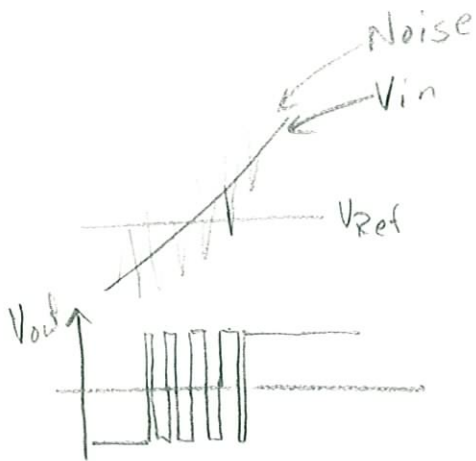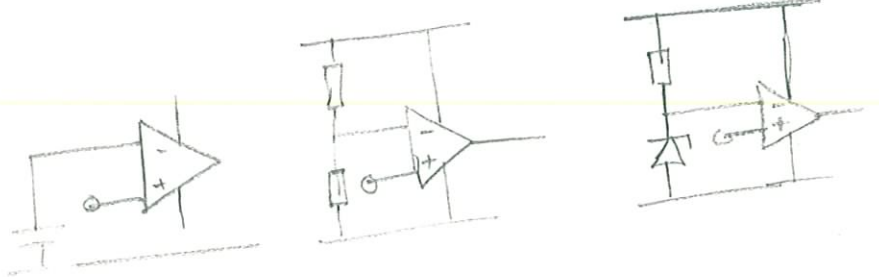- Voltage source
- Voltage divider
- Zener diode reference





Noise on the input gives a non-distinct transition.


Reduced with hysteresis

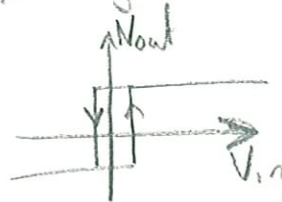

Implemented with positive feedback

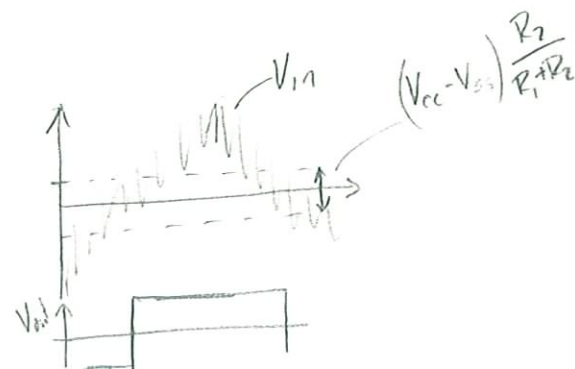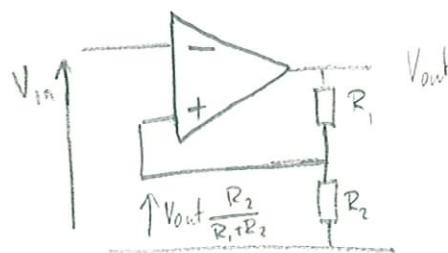

Summing amplifier

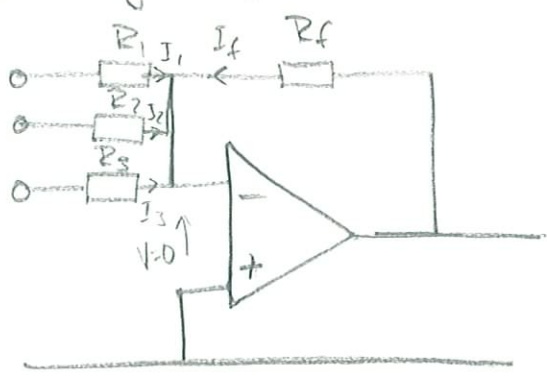

$$I_1 + I_2 + I_3 = -I_f$$


$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_{out}}{R_f}$$

$$V_{out} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots \right)$$

- Summing $R_1 = R_2 = R_3 = R$ $R_f = R$
- Summing with amp $R_f > R$
- Averaging $R_f = \frac{R}{3}$ or $\frac{R}{N}$
- Digital to Analog conv. $R_1 = \frac{R_2}{2} = \frac{R_3}{4} = R \dots$ $R_f = R$

An AD converter with previous design requires largely varying resistor values which is difficult realizing in ICs.

R/2R Ladder DAC

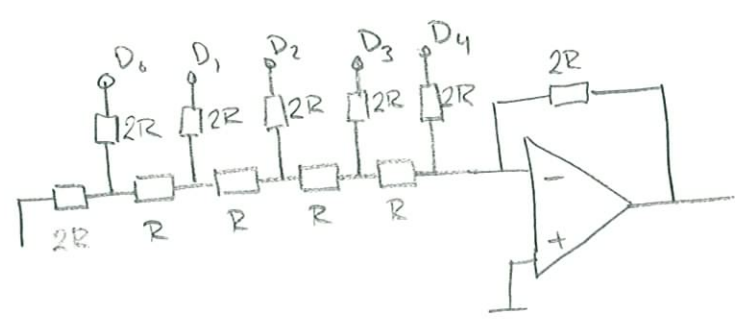


Instrumentation amplifier

Differential signals is often used in measurement system as electromagnetic disturbances affets both wires similar.



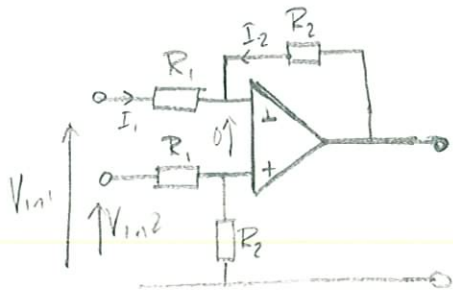Instrumentation amplifier
 - Controlable gain
 - Large CMRR




$$V_+ = V_{in2} \frac{R_2}{R_1 + R_2}$$

$$\frac{V_{in1} - V_+}{R_1} = -\frac{V_{out} - V_+}{R_2}$$

$$V_{out} = \frac{R_2}{R_1} (V_+ - V_{in1}) + V_+ = V_+ \left(1 + \frac{R_2}{R_1}\right) - V_{in1} \frac{R_2}{R_1}$$

$$V_{out} = V_{in2} \frac{R_2}{R_1 + R_2} \frac{R_1 + R_2}{R_1} - V_{in1} \frac{R_2}{R_1} = \frac{R_2}{R_1} (V_{in2} - V_{in1})$$

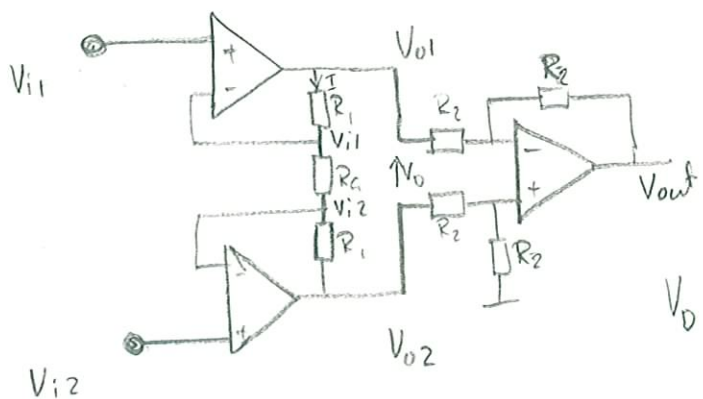- Slight variations in resistor values ruins CMRR
- Different input impedance for pos and negative input



$$I = \frac{V_{i1} - V_{i2}}{R_1}$$


$$V_{o1} = V_{i1} + R_1 I$$

$$V_{o2} = V_{i2} - R_1 I$$

$$V_D = V_{o1} - V_{o2} = V_{i1} - V_{i2} + 2R_1 I = (V_{i1} - V_{i2}) \left(1 + 2 \frac{R_1}{R_2}\right)$$

When $V_{i1} = V_{i2} \Rightarrow I = 0 \Rightarrow V_{o1} = 0 \Rightarrow$ Good common mode suppression

Integrator

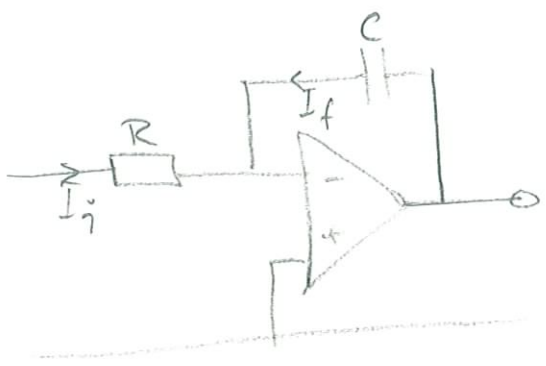

Capacitor


$$I = \frac{dQ}{dt} = C \cdot \frac{dV}{dt}$$

$$I_i = -I_f$$


$$\frac{V_{in}}{R} = -C \cdot \frac{dV_{out}}{dt}$$

$$\frac{dV_{out}}{dt} = -\frac{1}{RC} V_{in}$$
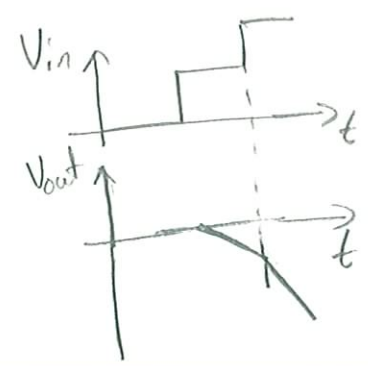
$$V_{out} = -\frac{1}{RC} \int_0^t V_{in} dt$$




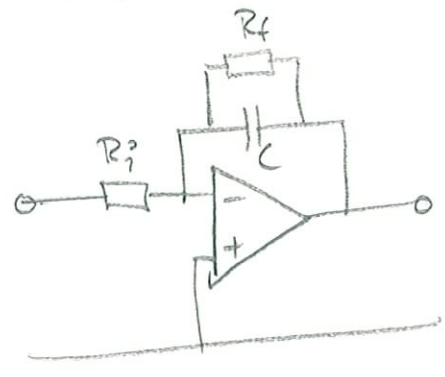Purely capacitive feed-back
 -I_{Bias} will be integrated



$R_f \gg R_i$ can overcome this issue
 without affecting the signal significantly.

Differentiator

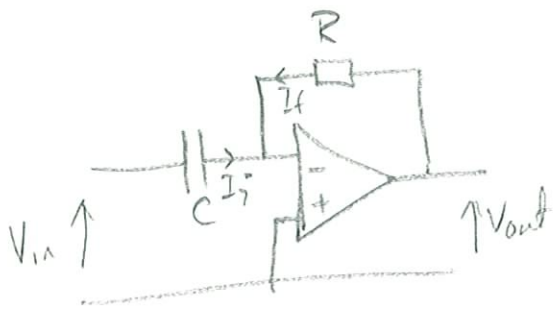

$$I = \frac{dQ}{dt} = C \cdot \frac{dV}{dt}$$

$$I_i = -I_f$$

$$C \cdot \frac{dV_{in}}{dt} = - \frac{V_{out}}{R}$$

$$V_{out} = -RC \cdot \frac{dV_{in}}{dt}$$

Charge sensitive amplifier


In measurement using a photodiode for detection of total accumulated photon flux or energy in a single photon the charge needs to be measured.

$$Q = \int I dt$$


$$I_i = -I_f = -C \frac{dV_{out}}{dt}$$

$$dV_{out} = -\frac{1}{C} I_i dt$$

$$V_{out} = -\frac{1}{C} \int I_i dt$$

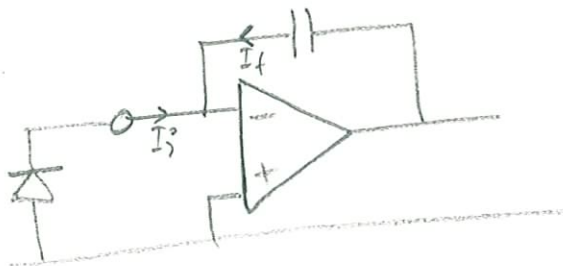


Needs to be resettable

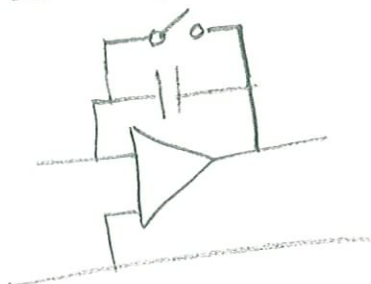

Current to Voltage converter


Photodiode, Current \propto Photon flux

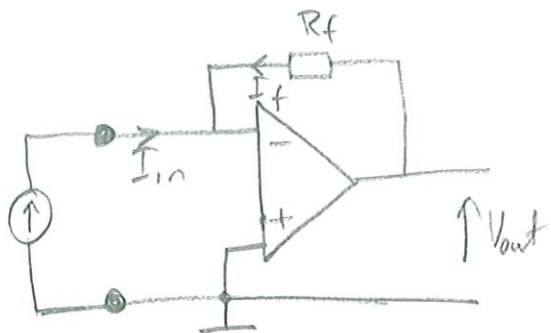

$$I_{in} = -I_f = -\frac{V_{out}}{R}$$

$$V_{out} = -I_{in} \cdot R$$

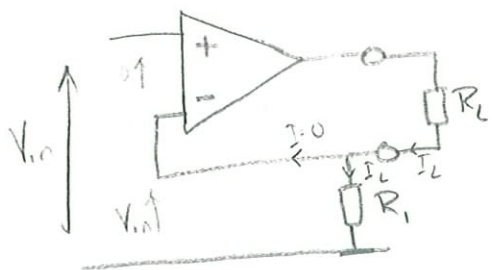
Voltage to current converter
(Current source)



$$V_{in} = R_1 \cdot I_L$$

$$I_L = \frac{V_{in}}{R_1} \text{ (Independent of } R_L \text{)}$$

Logarithmic amplifier

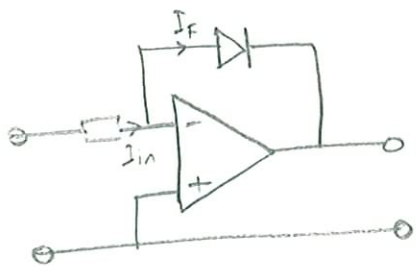

Diode equation: $I_0 = I_R e^{\frac{qV}{kT}}$


$$I_{in} = I_F =$$

$$\frac{V_{in}}{R_{in}} = I_R e^{\frac{-qV_{out}}{kT}}$$

$$\ln \frac{V_{in}}{R_{in} I_R} = \frac{-qV_{out}}{kT}$$

$$V_{out} = -0.026 \ln \left(\frac{V_{in}}{R_{in} I_R} \right)$$

Antilogarithmic amplifier

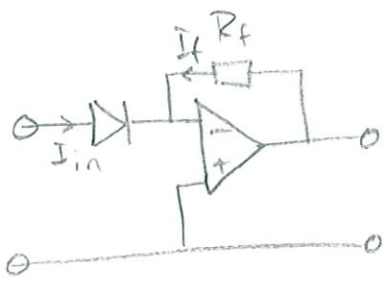


$$I_{in} = -I_f$$


$$I_{RE} e^{\frac{qV_{in}}{kT}} = -\frac{V_{out}}{R_F}$$

$$V_{out} = -R_F \cdot I_{RE} e^{0.026 V_{in}}$$


Driving large currents

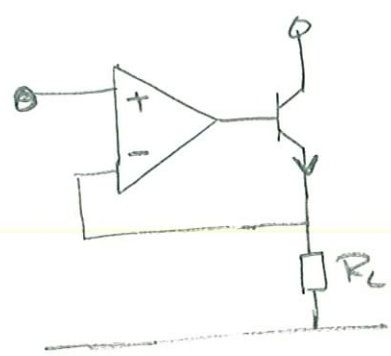

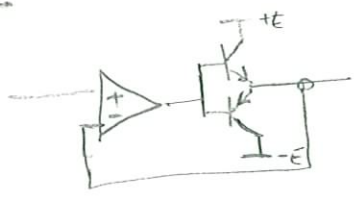
- The feed-back linearizing the non-linear performance of the transistor
- The OP-Amp only needs to drive $I_B \ll I_{RL}$




Peak detector

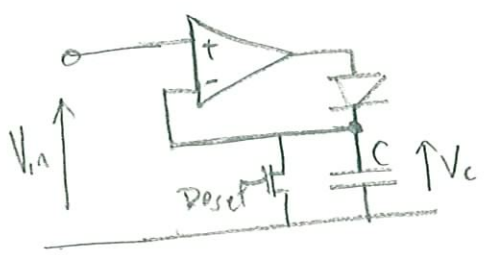

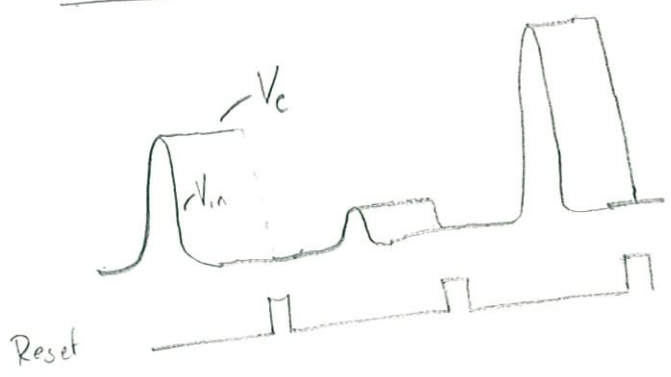As long as $V_{in} > V_c$ the capacitor charges to $V_c = V_{in}$
 As $V_{in} < V_c$ the capacitor is discharged very slowly.




Oscillators

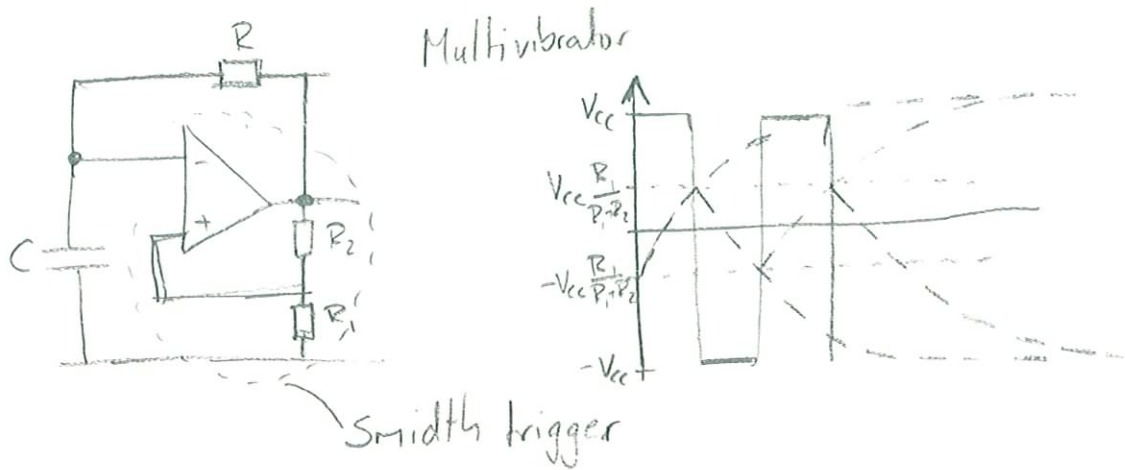

$$f \approx \frac{1}{2RC \ln \frac{2R_1 + R_2}{R_2}}$$

Conditions for oscillation

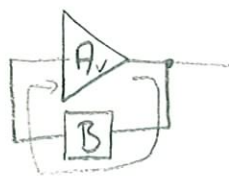- Phase shift around the loop should be 0°
- The voltage gain around the closed loop should be 1.





$$-\phi = 0^\circ$$

$$-A_{cl} = A_v \cdot B = 1$$

Wien-Bridge oscillator

- RC-Oscillator
- Suitable up to 1 MHz

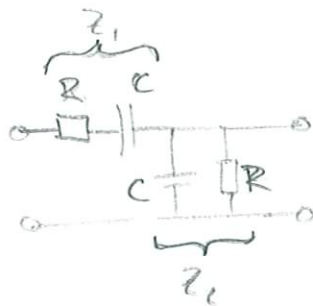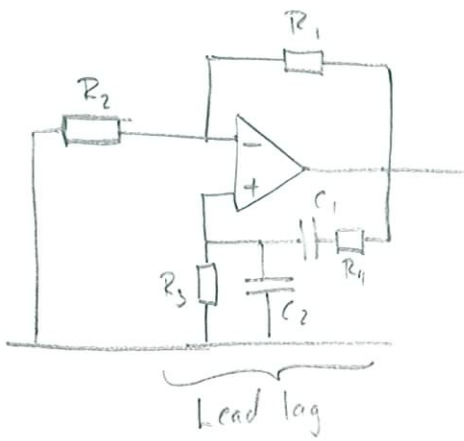


$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{R}{R + \frac{1}{j\omega C} + \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}}$$

$$\frac{R}{R + R + R + j\left(\omega RC - \frac{1}{\omega C}\right)} = \frac{R}{R\left(3 + j\left(\omega RC - \frac{1}{\omega C}\right)\right)} = \frac{1}{3 + j\left(\omega RC - \frac{1}{\omega C}\right)}$$

When $\omega RC - \frac{1}{\omega C} = 0$ $H(\omega) = \frac{1}{3}$ (-9.5 dB)

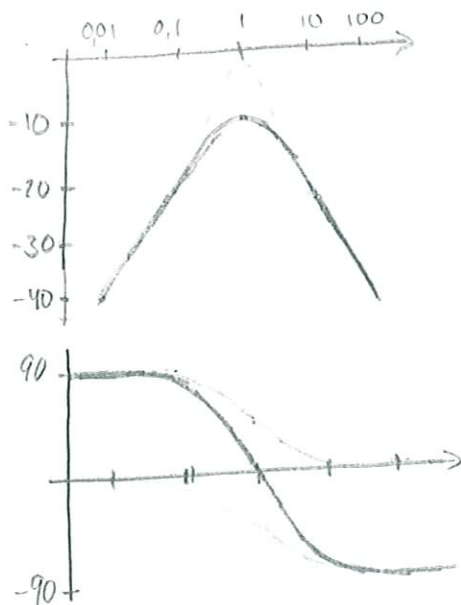$\omega RC = \frac{1}{\omega C} \implies \omega = \frac{1}{RC}$



$H(\omega) = \frac{1}{3}$ with $\phi = 0$ on V^+


Need $H(\omega) \approx 3$

R_1 & R_2 forms a non-inverting amplifier

$A_v = \frac{R_1 + R_2}{R_2}$ choose $\frac{10k + 22k}{10k} = 3.2$ times

Amplitude stabilization

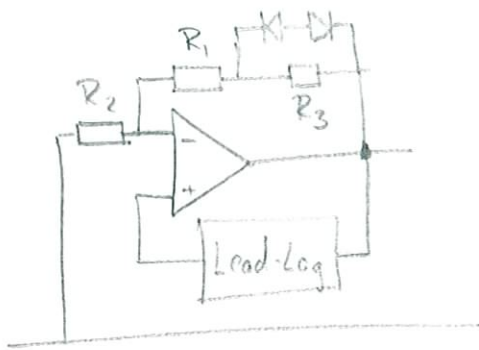- A_v needs to be > 3 for startup and be reduced to 3 at a specific amplitude.



Small amplitudes



$$A_v = \frac{R_1 + R_2 + R_3}{R_2}$$

Larger amplitudes

$$A_v = \frac{R_1 + R_2}{R_2}$$

Active filters

Active filters

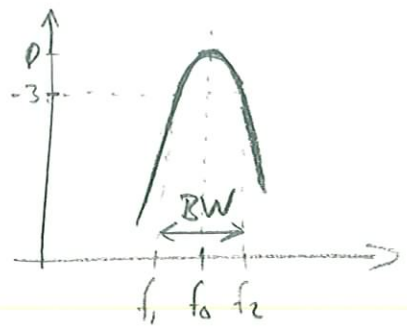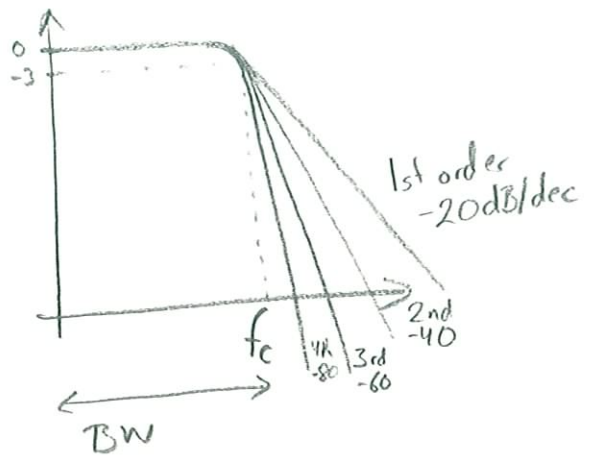

Quality factor

$$Q = \frac{f_0}{BW}$$



$$BW = f_{c2} - f_{c1}$$

$$f_0 = \sqrt{f_{c1} \cdot f_{c2}}$$


Filter response characteristics

- Higher order filters can be tailored depending on situation
- Three main characteristics

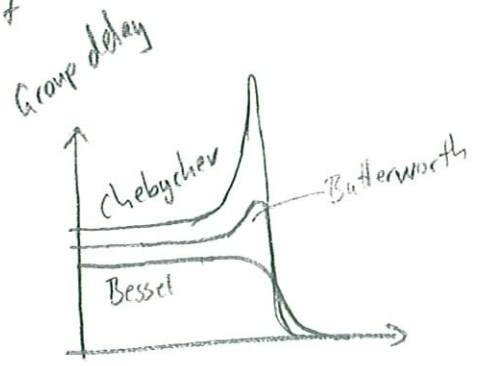
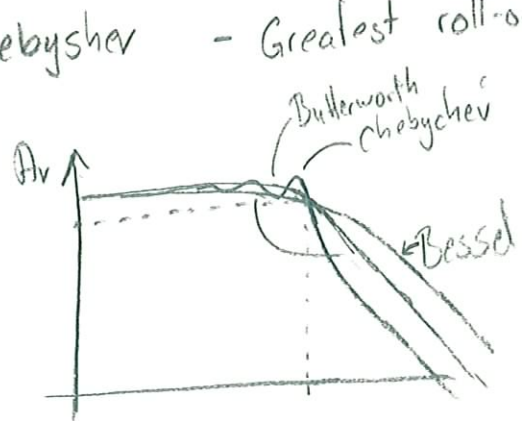
- Bessel - Linear phase (Minimum distortion, delay circuit)
- Butterworth - Maximally flat gain response
- Chebyshev - Greatest roll-off



General active filter

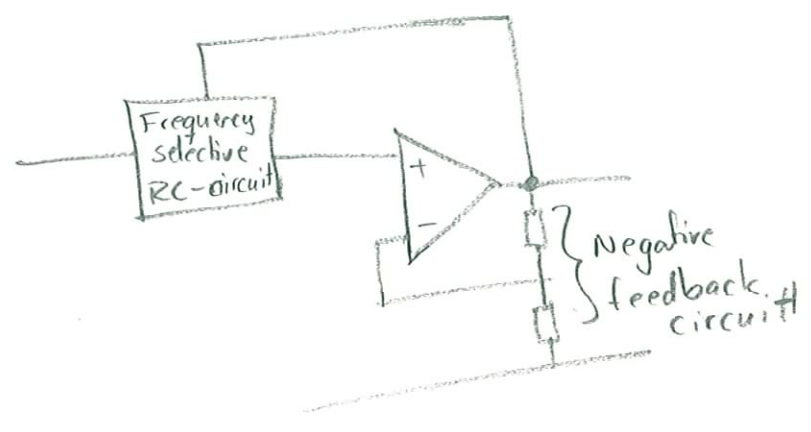

First order

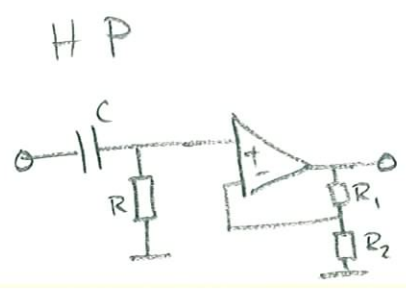
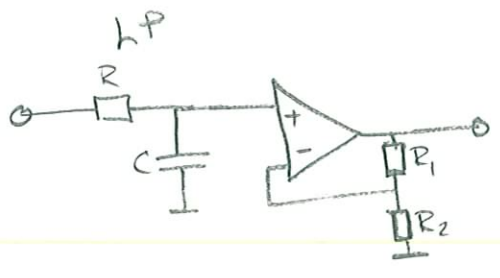


Second order filters


Two major topologies

- Sallen Key
- Multiple feedback


Sallen Key

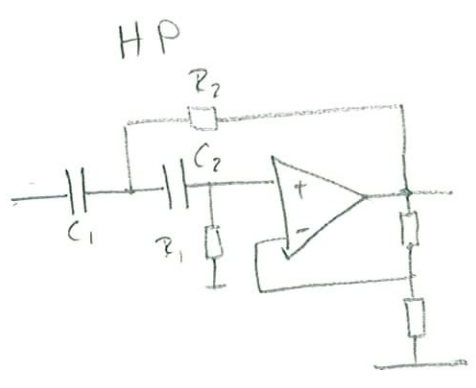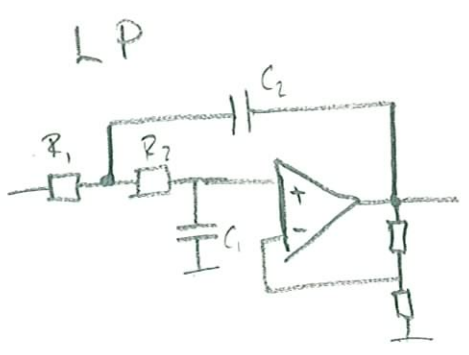

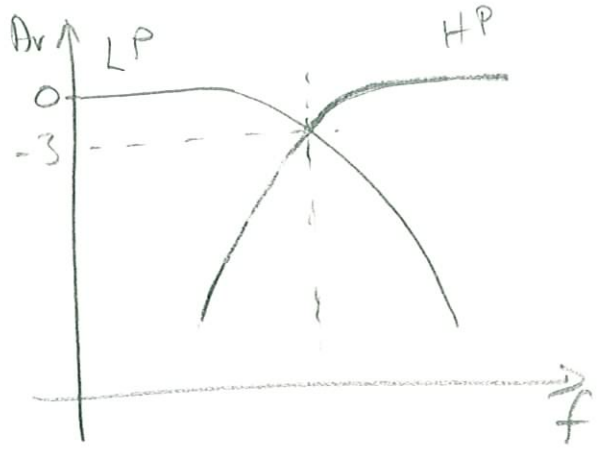- Resistor and capacitance values are calculated with help from tabulated values
- By swapping components in a LP filter to a HP configuration a HP-filter with same parameters are achieved




BP

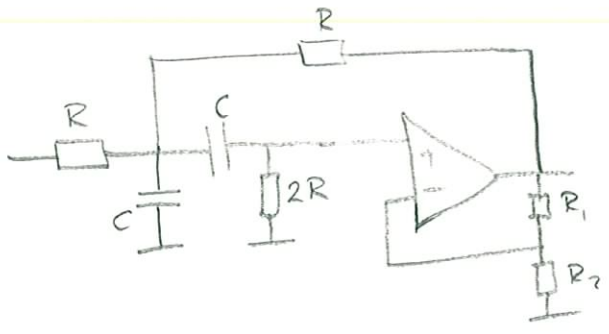


Multiple feed-back
 ⇒ often used in applications requiring high Q and high gain.


LP

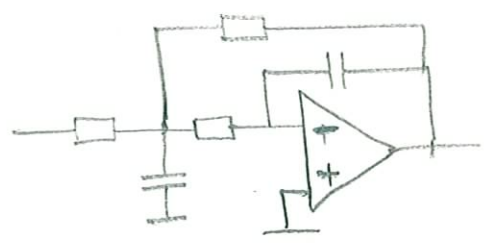

HP

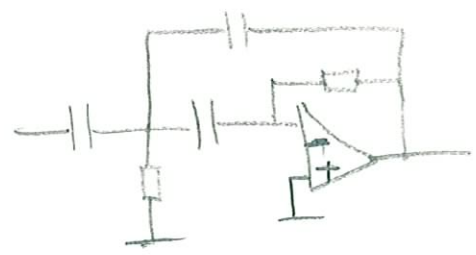

BP

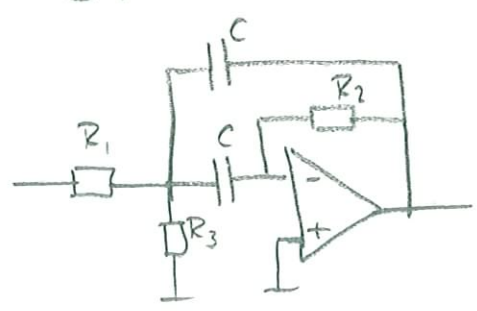

⇒ Higher order filters is achieved by cascading 2nd order filters

