

1a) I en linjär regulator är $I_{in} = I_{out}$ samt $V_{out} < V_{in}$ vilket ger en effektförlust på $P_{loss} = I(V_{in} - V_{out})$


b) $R_{in} = \infty$
 $R_{out} = 0$
 $A_v = \infty$
 $I_{in} = 0$
 $V_{in-diff} = 0$

c) 1. CE with bypassed R_E

d) 3. CC


e) 1. CE with bypassed R_E

f) 3. CC

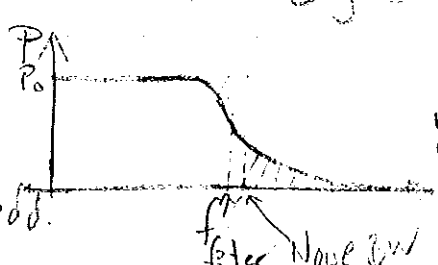
g) Brusbandbredd är den ekvivalenta bandbreddet bruset verkar om man tänker sig ett oändligt brant filter istället.
 Alltid lite större än filterets bandbredd.


$$\int_0^{BW_N} (P_0 - P) = \int_{BW_N}^{\infty} P$$

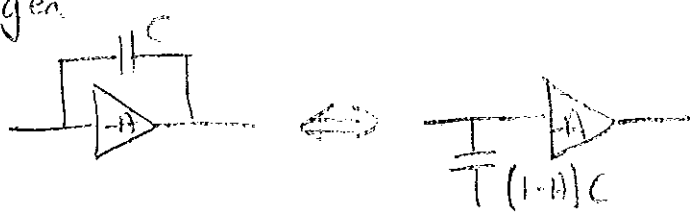h) En kapacitans mellan in och utgång på en inverterande förstärkare upplevs som "förstärkt" på ingången



2 a/

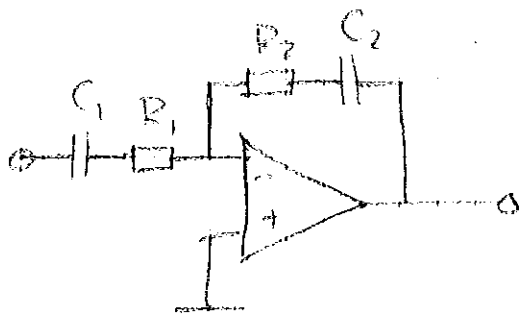

$$H_V = - \frac{Z_2}{Z_1} = - \frac{R_2 + \frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_1}} = - \frac{j\omega R_2 C_1 + \frac{j\omega C_1}{j\omega C_2}}{1 + j\omega R_1 C_1}$$



$$= - \frac{C_1}{C_2} \frac{1 + j\omega R_2 \frac{C_2}{C_1}}{1 + j\omega R_1 C_1} = - \frac{C_1}{C_2} \frac{1 + j\omega R_2 C_2}{1 + j\omega R_1 C_1}$$

$$= - \frac{C_1}{C_2} \frac{1 + j \frac{\omega}{\omega_2}}{1 + j \frac{\omega}{\omega_1}} = - \frac{C_1}{C_2} \frac{1 + j \frac{f}{f_2}}{1 + j \frac{f}{f_1}}$$


daer $f_1 = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi \cdot 40 \cdot 40 \cdot 10^{-9}} = 100 \text{ kHz} \quad (-1 \text{ BP})$

$f_2 = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi \cdot 40 \cdot 10^3 \cdot 4 \cdot 10^{-9}} = 1 \text{ kHz} \quad (+1 \text{ BP})$

b/

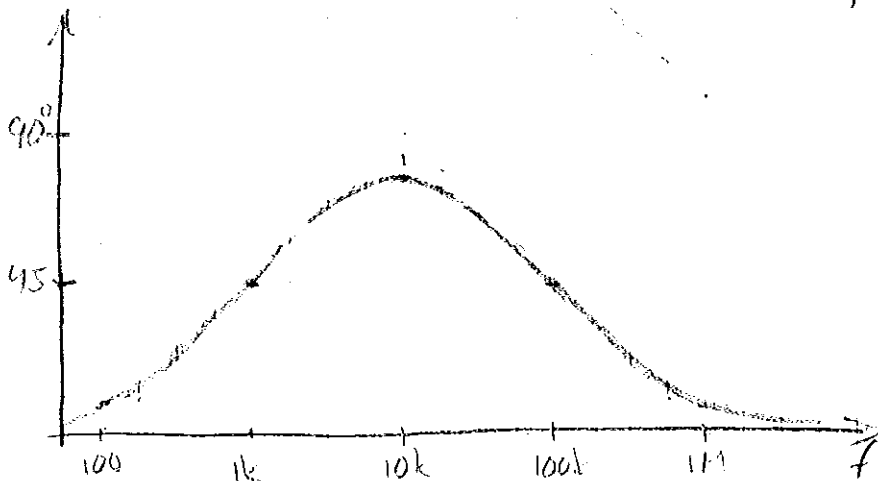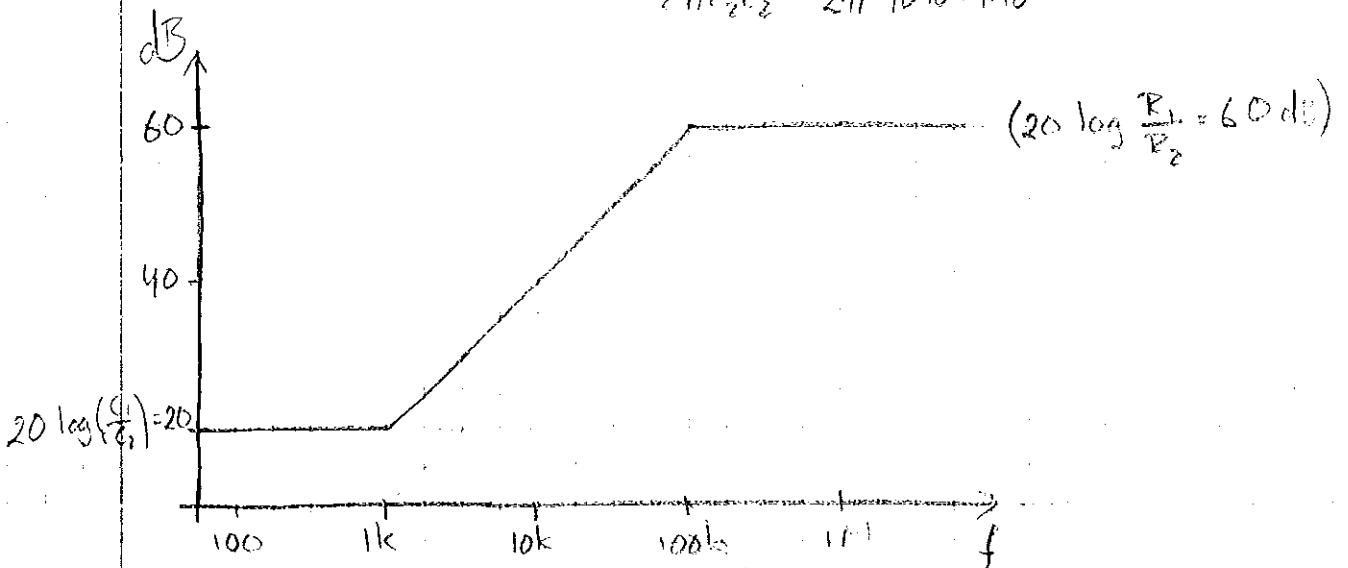

3a)

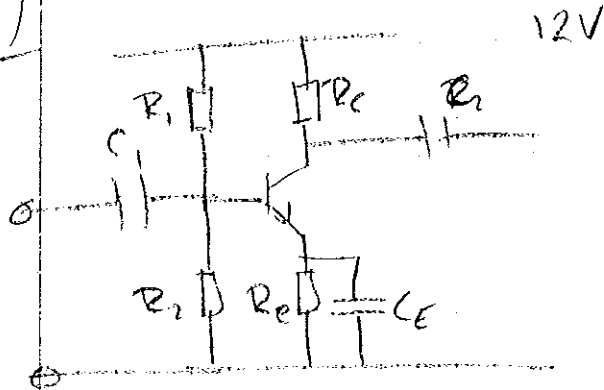


b)

$$R_{in} = R_1 // R_2 // R_{\pi}$$

$$R_{out} = R_c // R_o$$

$$A_v = \frac{v_{out}}{v_{in}} = -\beta \cdot I_b \cdot (R_c // R_o) \cdot \frac{1}{I_b \cdot R_{\pi}}$$

$$= -g_m (R_c // R_o)$$

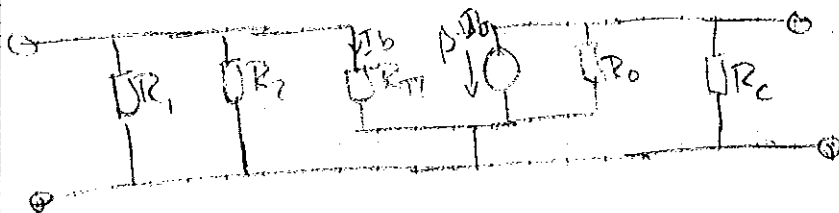

c) Set $V_{R_c} = 5V$ $V_{R_e} = 2V$ $V_{CE} = 5V$

$$R_{out} = R_c // r_o \quad \text{Select } R_c = 500 \Omega$$

$$\Rightarrow I_c = \frac{V_{R_c}}{R_c} = \underline{\underline{10 \text{ mA}}}$$

$$I_e = I_c \Rightarrow R_e = \frac{V_{R_e}}{I_c} = \frac{2}{10 \text{ mA}} = \underline{\underline{200 \Omega}}$$

$$I_c = 10 \text{ mA}, \quad V_{CE} = 5V$$

$$\text{Data sheet} \Rightarrow r_{\pi} \approx 3,5 \text{ k} \quad \beta \approx 600$$

$$I_B = \frac{I_c}{\beta} = \frac{10 \text{ mA}}{600} = 17 \mu\text{A}$$

$$\text{Select } I_{R_2} = 400 \mu\text{A}$$

$$\Rightarrow V_{R_2} = V_{R_e} + 0,7 \Rightarrow R_2 = \frac{2,7}{500 \mu\text{A}} = 6,8 \text{ k}\Omega$$


$$R_1 = \frac{12 - 2,7}{500 \mu\text{A}} = \frac{9,3}{500 \mu\text{A}} = 23 \text{ k}\Omega$$

$$R_{in} = R_1 // R_2 // R_{\pi} = \frac{1}{\frac{1}{6,8k} + \frac{1}{23k} + \frac{1}{3,5k}} = 2,1k \Omega$$

$$R_{out} = R_c // R_o = \frac{500 \cdot 10k}{500 + 10k} = 480 \Omega$$

$$A_v = \frac{\beta_{ac}}{r_{\pi}} (R_c // r_o) = \frac{600}{3,5k} \cdot 480 = 82,9$$


4a)

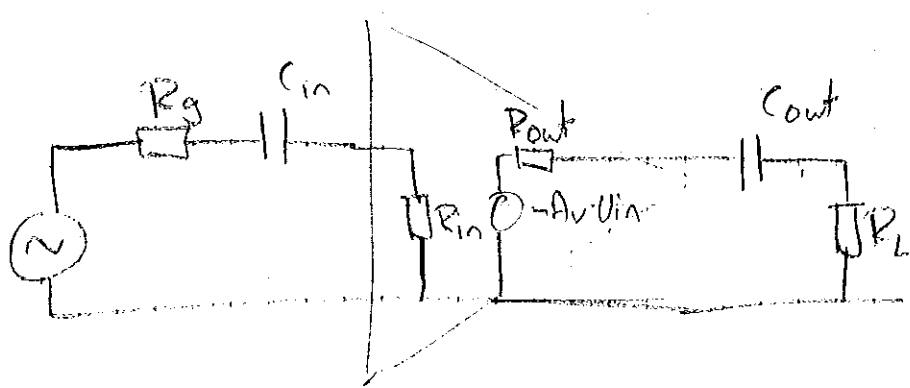

b)

$$U_{out,peak} = U_{in} \cdot A_{v0} \cdot \frac{R_{in}}{R_{in} + R_g} \cdot \frac{R_L}{R_{out} + R_L} = 1m \cdot 82 \cdot \frac{2,1k}{500 + 2,1k} \cdot \frac{2k}{480 + 2k} = 53mV$$

c)

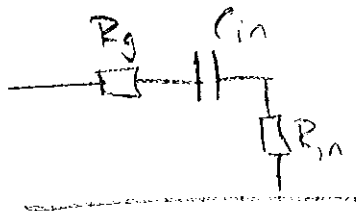


$$f_g = \frac{1}{2\pi(R_g + R_{in})C_{in}} = 20Hz$$

$$C_{in} = \frac{1}{2\pi(500 + 2,1k)20} = 3,1\mu F$$

pss $C_{out} = \frac{1}{2\pi(480 + 2k)20} = 3,2\mu F$

$$C_E = \frac{1}{2\pi(R_{eff} \parallel \frac{1}{g_m})f_c} = \frac{1}{2\pi \cdot 5,7 \cdot 20} = 1,4\mu F$$
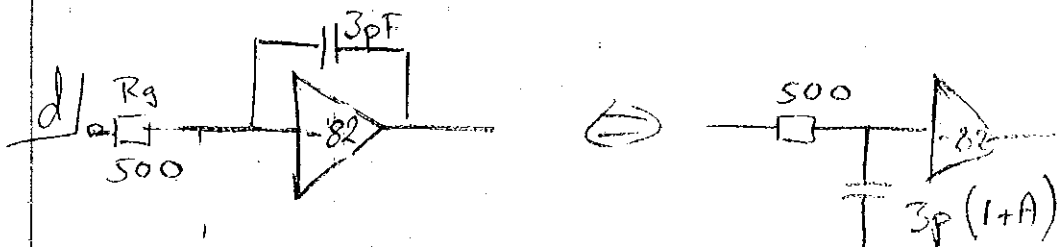
$$\frac{200 \cdot \frac{3,5k}{600}}{200 + \frac{3,5k}{600}} = 5,7\Omega$$






$$f_{Miller} = \frac{1}{2\pi R_g C_{Miller}} = \frac{1}{2\pi \cdot 500 \cdot 249 \cdot 10^{-12}}$$

$$= 1,3MHz$$

$$3p \cdot 83 = 249pF$$

5a)

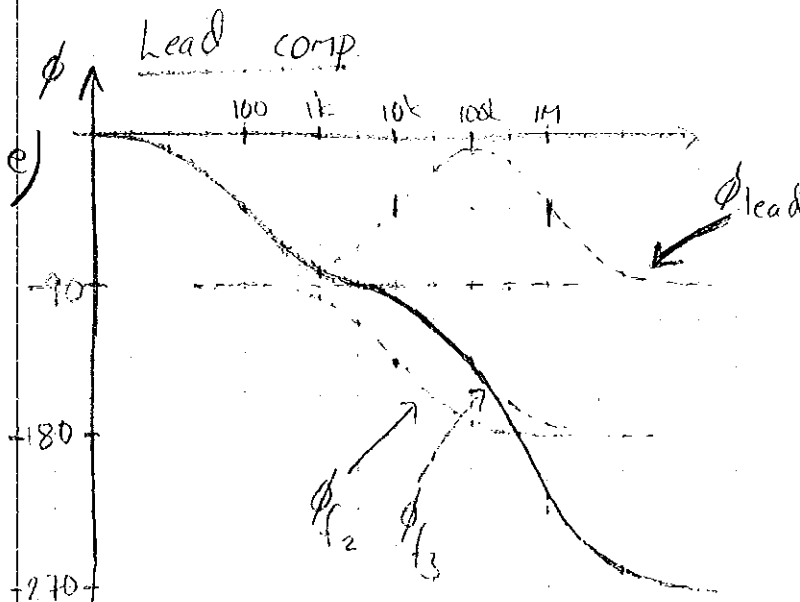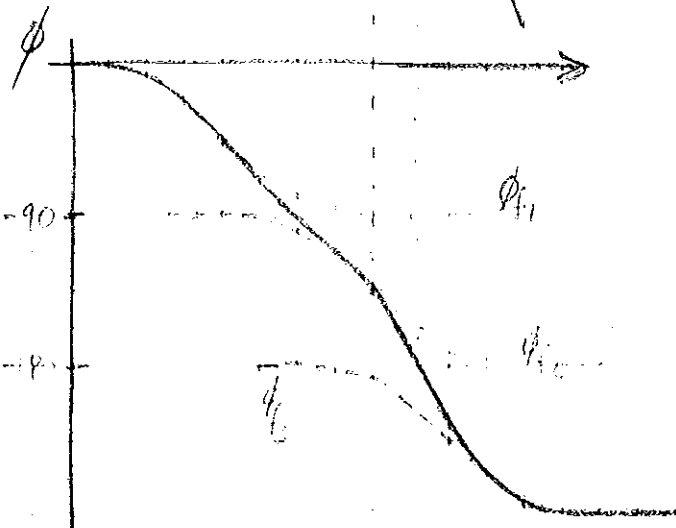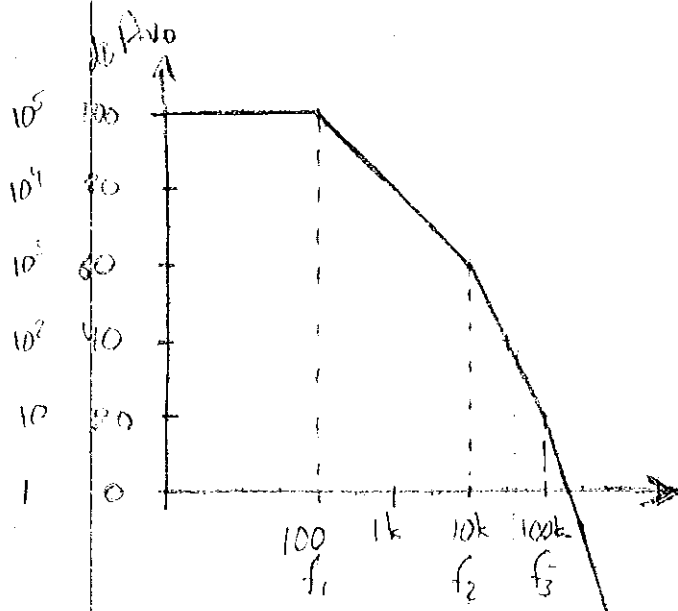

b) For stable operation without compensation the gain must be reduced so that $\beta \cdot A_{vo} = 0 \text{ dB}$ when $\phi = -135^\circ$ that is $\beta = -60 \text{ dB}$ or 10^{-3} which gives $\beta \cdot A_{vo} = 40 \text{ dB}$

\Rightarrow phase margin $= -45^\circ$

c) Gain
 $< 38 \text{ dB}$ Unstable
 $38 - 60 \text{ dB}$ $\phi_m < 45^\circ$
 $> 60 \text{ dB}$ Stable

$$f_{\text{lead1}} = f_2 = 10 \text{ k}$$

$$\beta \cdot A_{vo} = 60 \text{ dB}$$

$$\Rightarrow \beta = -40 \text{ dB}$$


Lead filter drops with -20 dB/decade .

For $\beta = -40 \text{ dB}$ two decades can differ between

f_{lead1} and f_{lead2} .

$$f_{\text{lead2}} = 100 \cdot f_{\text{lead1}} = 1 \text{ MHz}$$

f)

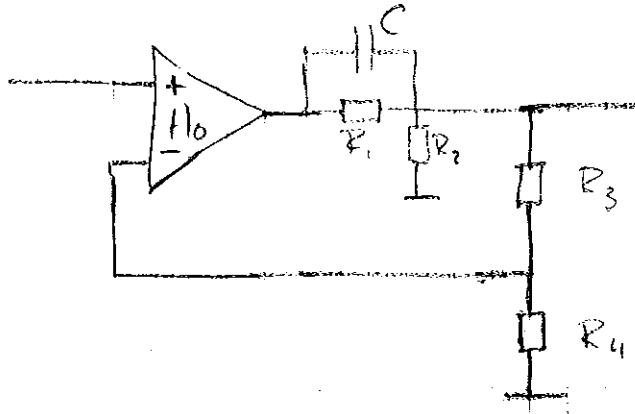

$$f_{lead} = 10k = \frac{1}{2\pi R_1 C}$$

$$f_{2lead} = 1MHz = \frac{1}{2\pi (R_1 // R_2) C}$$

$$\text{Löt } R_1 = 10k \Rightarrow C = \frac{1}{2\pi \cdot 10k \cdot 10^4} = 16 \text{ nF}$$

$$\Rightarrow R_1 // R_2 = \frac{1}{2\pi \cdot 1 \cdot 10^6 \cdot 16 \cdot 10^{-9}} = 99,5 k$$

$$\Rightarrow R_2 = 100 \Omega \Rightarrow R_1 // R_2 = 99,5 \Omega$$

20 dB gain \Leftrightarrow 10 times

$$A_v = \frac{R_3}{R_3 + R_4}$$

$$\text{Löt } R_3 + R_4 = 100k \quad (D_{vs} \gg R_1)$$

$$\Rightarrow R_3 = 10k \Omega \quad \text{or} \quad R_4 = 90k \Omega$$

$$\text{ger } A_v = 10 = 20 \text{ dB}$$