

1 a) In a linear regulator the current is equal before and after the regulator but the voltage is reduced giving an efficiency $\eta = \frac{P_{out}}{P_{in}} = \frac{U_{out} \cdot I_{out}}{U_{in} \cdot I_{in}} = \frac{U_{out}}{U_{in}}$


In a switched regulator the current $I_{in} = I_{out}$ is increased when the voltage is reduced.

- b)
- $R_{in} = \infty$
 - $R_{out} = 0$
 - $A_{v0} = \infty$
 - $I_{in} = 0$
 - $V_{indiff} = 0$


c) The noise bandwidth of a non-ideal filter is the bandwidth of an ideal filter which will pass the same noise power as the non-ideal filter.

$$BW_N > BW_{-3dB} \quad (BW_N = 1.57 \cdot BW_{-3dB} \text{ for a 1st order filter})$$

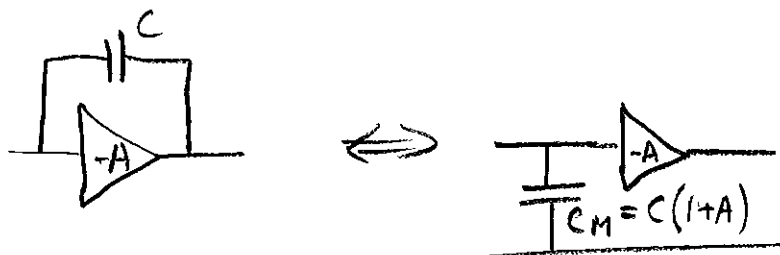d) A capacitor connected between the input and output of an inverted amplifier behaves like an larger amplifier connected at the input.



21

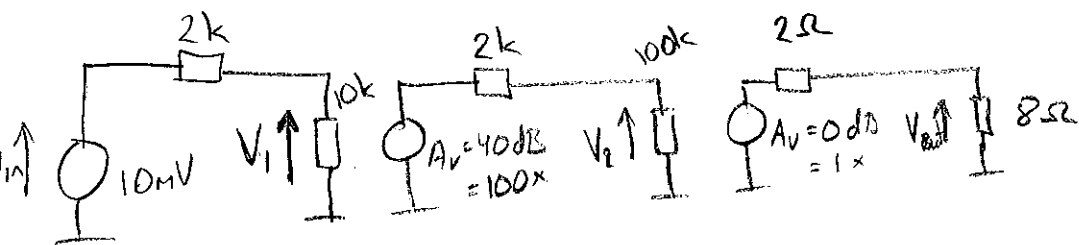


Voltage division

$$V_1 = V_{in} \frac{10}{10+2} = V_{in} \frac{10}{12}$$

$$V_2 = 100 \times V_1 \times \frac{100}{100+2} = 100 \cdot V_{in} \frac{10}{12} \frac{100}{102}$$

$$V_{out} = 1 \times V_2 \times \frac{8}{8+2} = 100 \cdot V_{in} \frac{10}{12} \frac{100}{102} \frac{8}{10} = 65 \cdot V_{in} = \underline{\underline{650 \text{ mV}}}$$

391

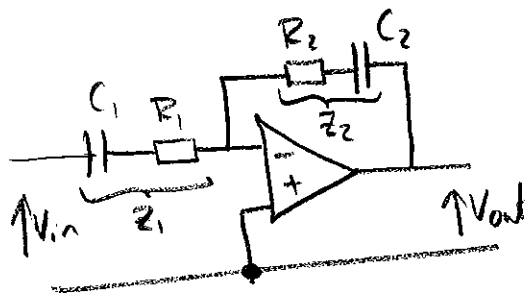

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$Z_2 = \frac{1 + j\omega R_2 C_2}{j\omega C_2}$$

$$H(\omega) = A_v = - \frac{Z_2}{Z_1} = - \frac{\frac{1 + j\omega R_2 C_2}{j\omega C_2}}{\frac{1 + j\omega R_1 C_1}{j\omega C_1}} = - \frac{C_1}{C_2} \frac{1 + j\omega R_2 C_2}{1 + j\omega R_1 C_1}$$



$$= - \frac{C_1}{C_2} \frac{1 + j \frac{f}{f_2}}{1 + j \frac{f}{f_1}}$$

$$f_2 = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi \cdot 40 \cdot 40n} = 10 \text{ kHz}$$


$$f_1 = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi \cdot 40k \cdot 4n} = 1 \text{ kHz}$$

$$\frac{C_1}{C_2} = \frac{40}{4} = 10 \quad (20 \text{ dB})$$

3 b)

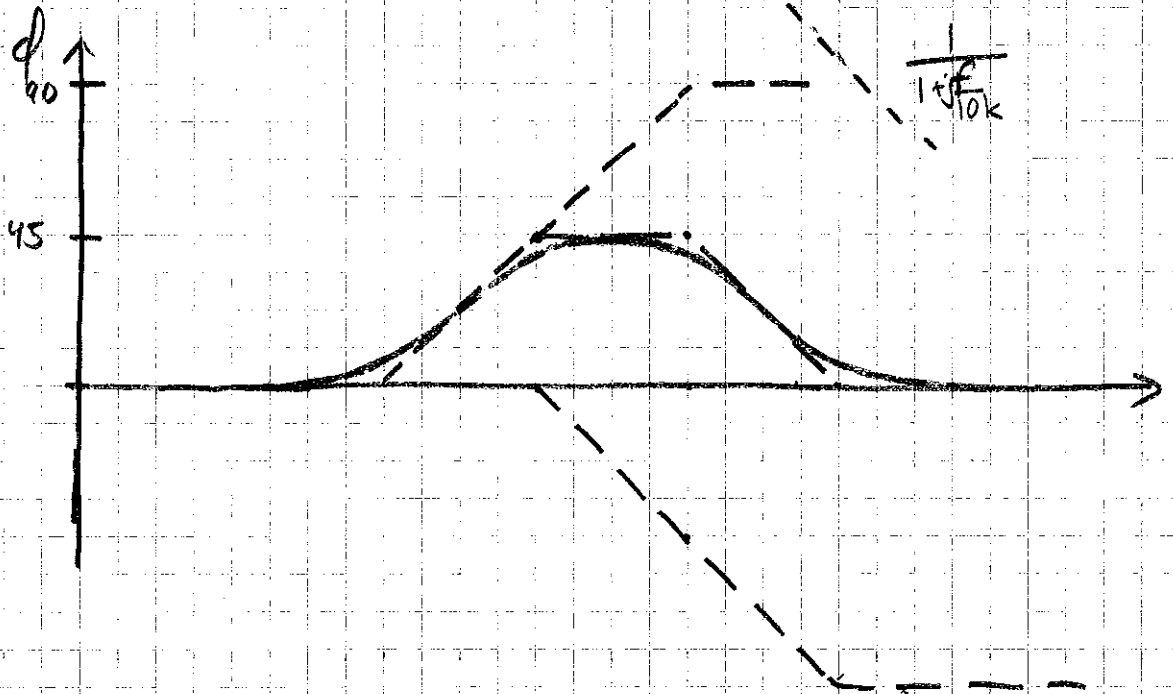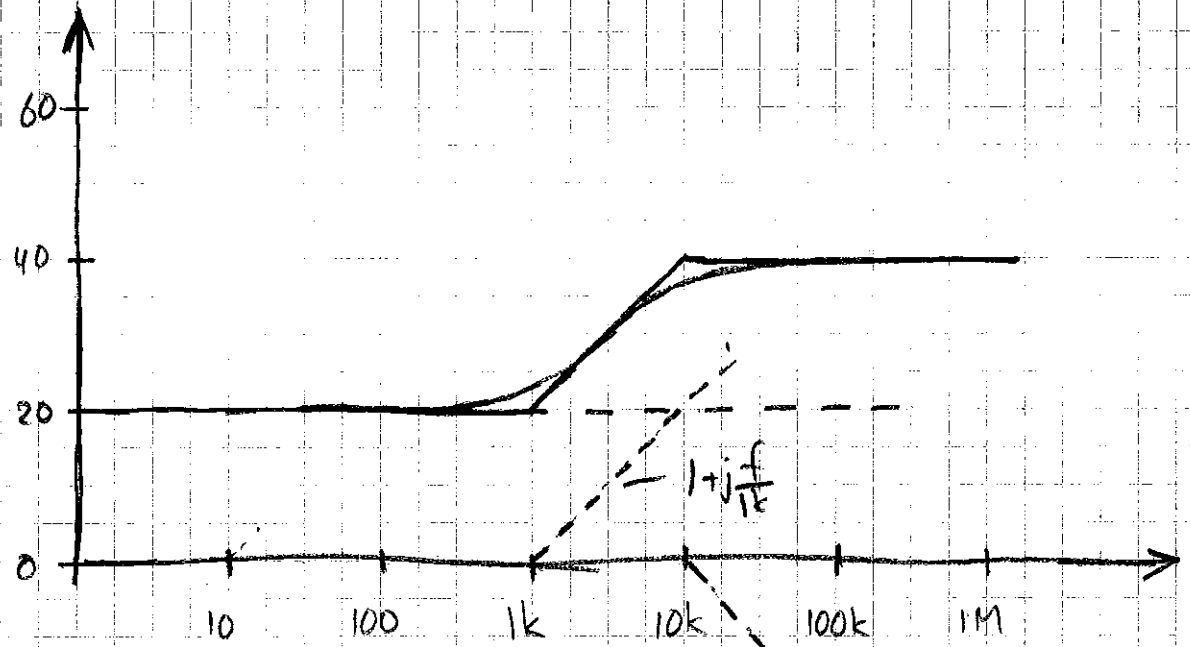

4

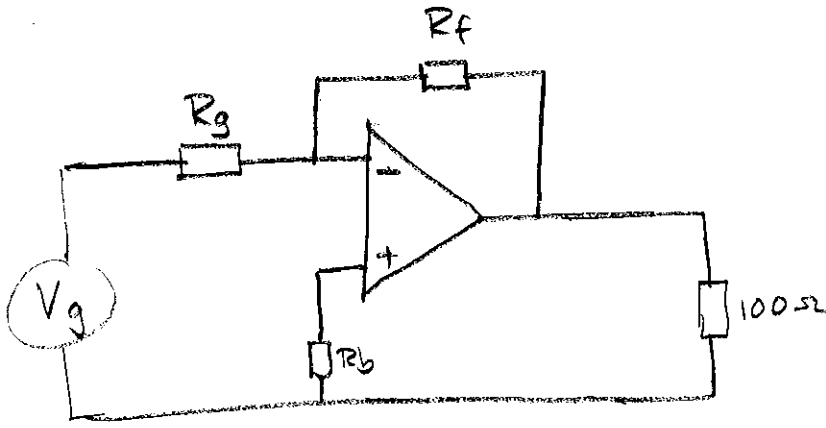

$V_g = 100 \mu V$ $A_v = -\frac{R_f}{R_g} = \frac{1k}{50} = 20 \text{ times}$ Fig 2, page 3 in data sheet


$\Rightarrow -3 \text{ dB @ } 100 \text{ MHz}$
 $\Rightarrow A_v = 10 \text{ times}$

$V_{out} = V_g \cdot A_v = 100 \mu V \times 10 = 1 \mu V$

a)

$P_{out} = V_{out} \cdot I_{out} = V_{out} \frac{V_{out}}{R_L} = \frac{V_{out}^2}{R_L} = \frac{1 \mu V^2}{100} = 10 \text{ nW}$

b)

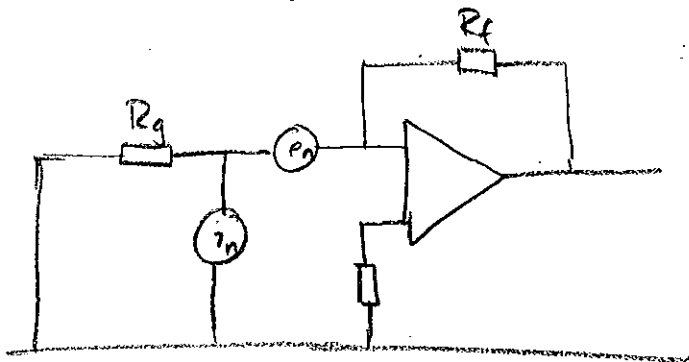

$$V_n = \sqrt{e_n + i_n \cdot R_g \left(4kTgR_g \right)} = \sqrt{\left(1,05 \cdot 10^{-9} \right)^2 + \left(1,6 \cdot 10^{-12} \cdot 50 \right)^2 + 16,4 \cdot 10^{-21} \cdot 50}$$

Ger inga poäng ovdrag

$= 1,38 \text{ nV}/\sqrt{\text{Hz}}$

$V_{noise out} = A_v \cdot V_n \cdot \sqrt{BW_N} = 20 \cdot 1,38 \cdot 10^{-9} \cdot \sqrt{100 \text{ MHz} \cdot 1,57}$

Bandwidth → Noise
 Fig 2, page 3 in data sheet
 Also in text page 6 data sheet

$= 350 \mu V$

$P_{noise out} = \frac{V_{noise out}^2}{R_L} = \frac{350 \cdot 10^{-6}^2}{100} = 1,2 \text{ nW}$

$$SNR = \frac{P_{out}}{P_{Noise_{out}}} = \frac{10 \text{ nW}}{1,2 \text{ nW}} = 8,3 \text{ times}$$


c) By filtering the amplifier to only cover the 100 MHz band with a BW of 5 MHz would not affect the signal but reduce the noise $\sqrt{\frac{100}{5}} = 4,5$ times

$$\Rightarrow SNR \simeq 8,3 \times 4,5 = 37 \text{ times}$$

(A low pass filter would be enough as the amplifier itself have a upper bandwidth of 100 MHz.

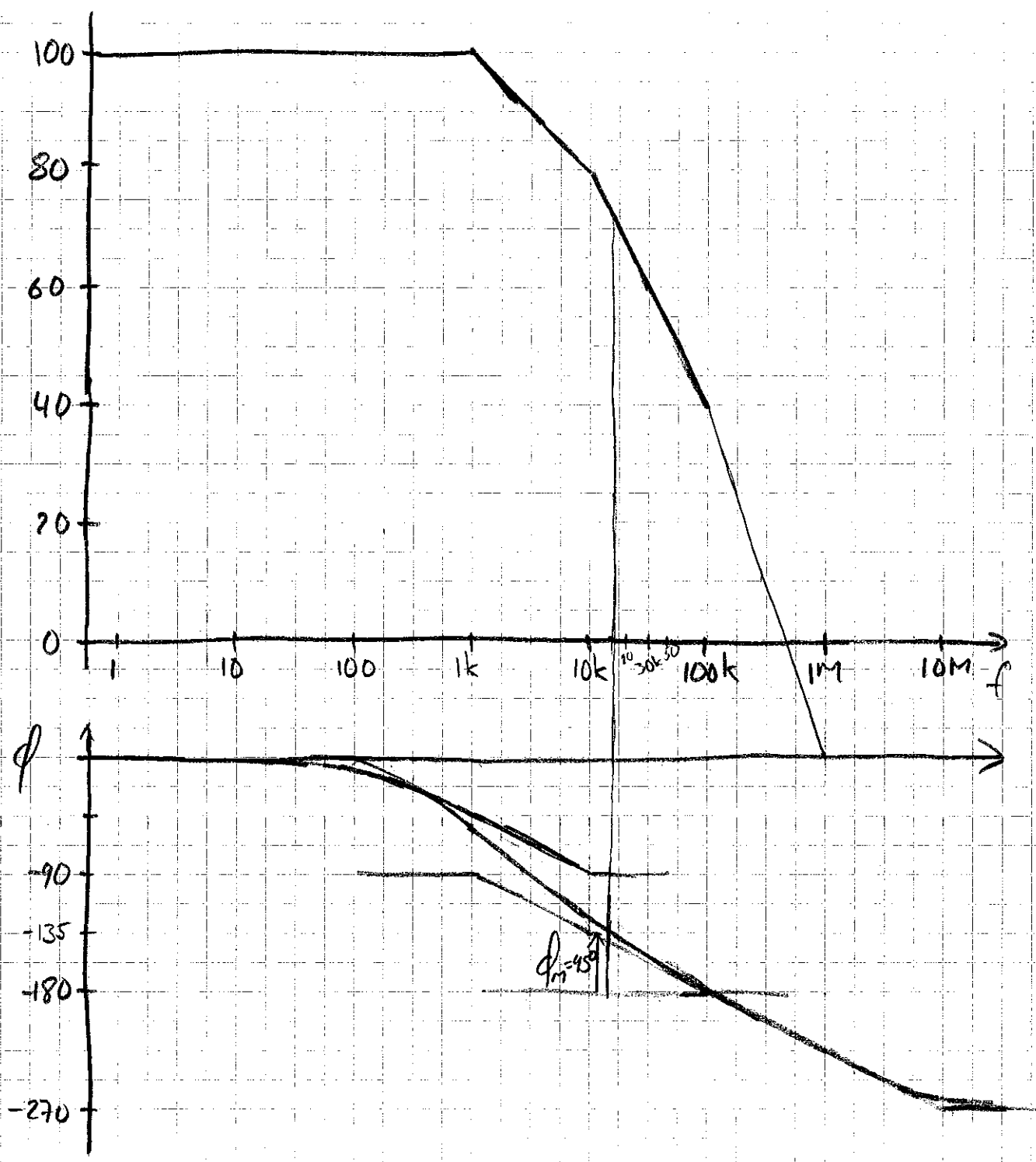5) a)

$$A_{vo} = \frac{100\,000}{(1+j\frac{f}{1k})(1+j\frac{f}{10k})(1+j\frac{f}{1MHz})}$$



b $\phi_m = 45^\circ$ ($\phi = -135^\circ$) @ approx 15 kHz

This is the highest frequency the amplifier can be used as an amplifier.

c

B	A_v	
$0 - 2,5 \cdot 10^{-4}$	100 - 72 dB	Stable
$2,5 \cdot 10^{-4} - 0,01$	72 - 40 dB	Nearly stable
$0,01 - 1$	40 - 0 dB	Unstable


See separate bode diagrams

d $f_1 = 10$ kHz (2nd pole)

$f_2 = 1$ MHz (10x 3rd pole)

e See separate bode diagram

f

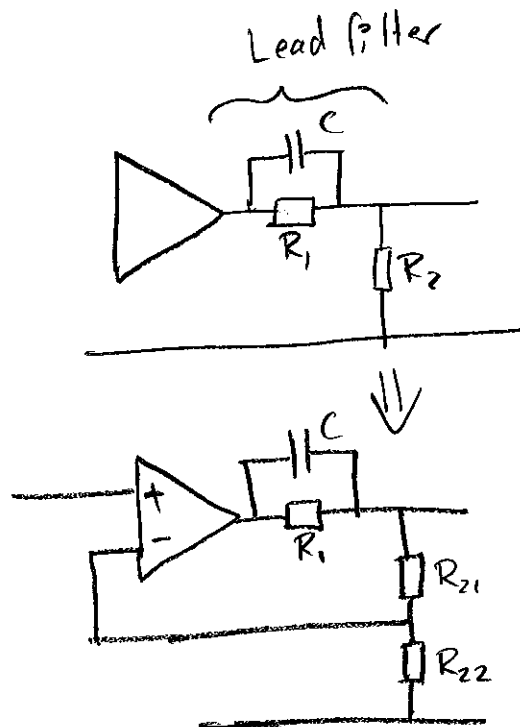

$A_{v0} \cdot \text{Filter}$

$$\frac{R_2}{R_1 + R_2} = 0,01 \quad R_1 = 100 \cdot R_2$$

Let $R_1 = 100$ k, $R_2 = 1$ k

$$f_1 = \frac{1}{2\pi R_1 C} \quad C = \frac{1}{2\pi f_1 \cdot R_1} = 160 \text{ pF}$$

20 dB amp (100 times)

$$B = 0,01 \left(= \frac{1}{A_v} \right)$$


Feed-back factor

Voltage division

$$B = \frac{R_{22}}{R_{21} + R_{22}} = 0,01 \Rightarrow R_{21} = 100 \cdot R_{22}$$


$$\text{But } R_{21} + R_{22} = R_2 = 1 \text{ k}\Omega$$
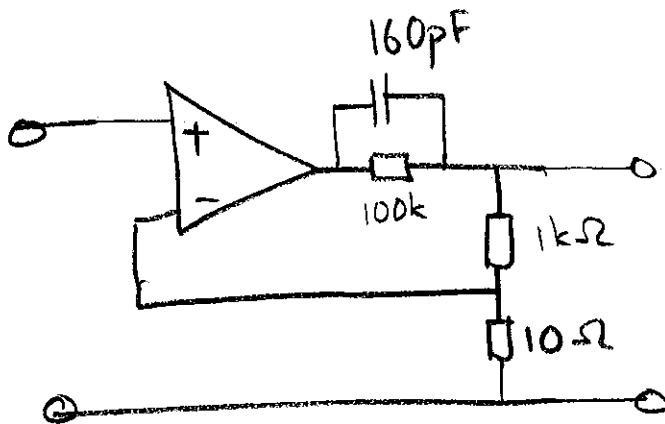
$$\Rightarrow R_{21} = 1 \text{ k}\Omega, R_{22} = 10 \Omega$$



5] c)
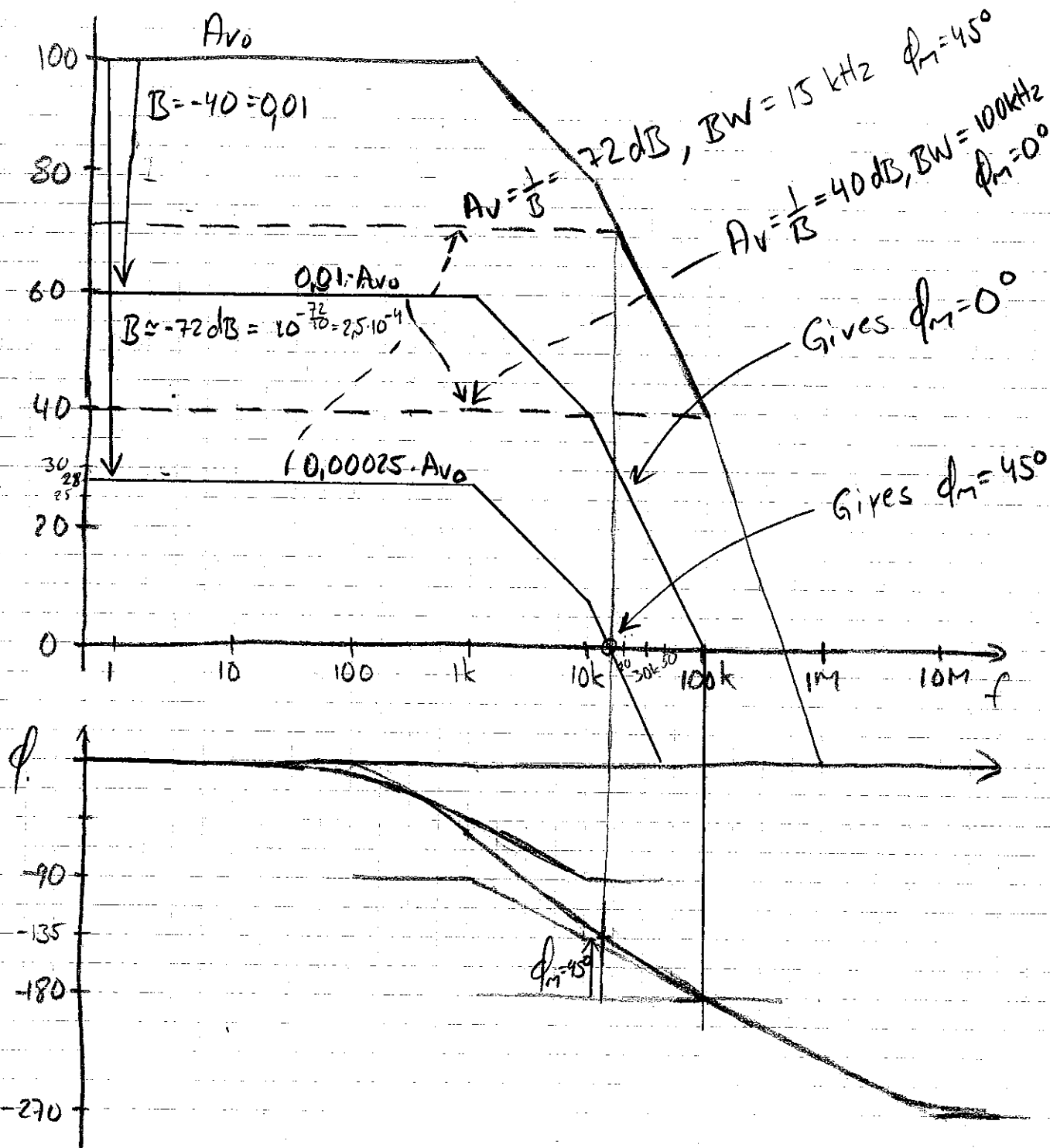
$$A_{vo} = \frac{100\,000}{(1+j\frac{f}{1k})(1+j\frac{f}{10k})(1+j\frac{f}{1MHz})}$$



5] e]

$$A_{v0} = \frac{100\,000}{(1+j\frac{f}{1k})(1+j\frac{f}{10k})(1+j\frac{f}{1MHz})}$$

